
	MECH 10 - Lab 08 Series / Parallel Circuits	 <i>Real Skills Real Jobs</i>
Name: Cayce Beames Date: October 1, 2019 Professor Steven Gillette		

Abstract

In this lab, I used several resistors, a Zener diode, a breadboard and a DC power supply to simulate combination series / parallel circuits as well as to understand the behavior of a Zener diode.

Because I missed this lab in class, I substituted resources from my home lab including an 830 connection-point breadboard, a UNI-T UTP3315TFL-II regulated DC power supply and a UNI-T UT89XD digital multimeter.

Learning Objectives

- Build series / parallel circuits as per a schematic diagram
- Measure electrical values using a digital voltmeter
- Use Ohm's Law to reduce a series /parallel circuit to the simplest form
- Use a data table and schematic diagrams to capture field measurements

Notes:

1. Take all voltage measurements relative to ground (unless otherwise stated)
2. Record relevant measurements and calculation results in data tables
3. Record all measured values on the circuit schematics
4. Use all available precision in calculations, round off answers to 3 significant figures

Materials

Quantity	Description
1	DC Power Supply
1	Digital multimeter (DMM)
1	Breadboard
Circuit 1 & 2	
1	R1, R2, R3, R4, R5, R6 – choose any resistors between 1K Ω and 5.6K Ω , each of different value
Circuit 3	
1	Zener diode, 1N4733A, 5.1V
1	R1 – 300 Ω
1	R2 – 470 Ω and 1k Ω

Procedure – Series / Parallel Circuits

Circuit 1

1. Selected resistors for circuit 1, 2 and 3 according to the materials chart above.
2. Built Circuit 1 *without the voltage source connected* (i.e. left the circuit power supply leads disconnected)

3. **Total Resistance (expected)** - Calculated and recorded R_{Texp} , the total circuit resistance using circuit reduction, expected resistor values and one of the R_{equiv} formulas.

	Series Resistor Value (Ω)		Branch Resistance (Ω)	Branch Conductance (g)	Expected Parallel Resistance (Ω)	Expected Total Resistance (Ω)
R1	1.00E+03	Branch 1	2.00E+03	500.00E-06	1.15E+03	2.15E+03
V _{source}	10.00E+00	Branch 2	2.70E+03	370.37E-06		

4. **Total Resistance (measured)** – Measured and recorded R_T and compared the measured value to the expected value using the % Error formula.

Expected Total Resistance (Ω)	Measured Total Resistance (Ω)	% Error
2.15E+03	2.16E+03	-0.3%


5. Set the power supply to 10V. Measured and recorded V_S , the power supply voltage to three significant figures.
6. **Circuit Currents (expected)** - Calculated and recorded I_T , I_{R2} , I_{R3} – expected circuit currents using Ohm's Law, V_S , and R_{Texp} values. Used Kirchoff's Law to show that total current equals the sum of the branch currents.

	Expected Current (Amp)
R ₁	4.65E-03
Branch 1	2.67E-03
Branch 2	1.98E-03

7. **Circuit Currents (measured)** Measured and recorded I_T , I_{R2} , I_{R3} , circuit current using the DMM as an ammeter. Recorded the values and compare measured to expected values using the % Error formula.

	Expected Current (Amp)	Measured Current (Amp)	% Error
R ₁	4.65E-03	4.61E-03	0.9%
Branch 1	2.67E-03	2.61E-03	2.4%
Branch 2	1.98E-03	1.99E-03	-0.5%

8. **Reduction schematic** – drew the circuit reduction steps for Circuit 1 on the Circuit Reduction Worksheet

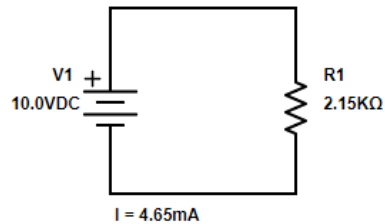

Circuit 2

9. Built circuit 2.
10. *Calculated and recorded* total resistance

	Series Resistor Values (Ω)		Branch Resistance (Ω)	Branch Conductance (g)	Expected Parallel Resistance (Ω)	Expected Total Resistance (Ω)
R1	1.00E+03	Branch 1	4.70E+03	212.77E-06	2.92E+03	8.92E+03
R6	5.00E+03	Branch 2	7.70E+03	129.87E-06		
V _{source}	10.00E+00					

11. *Measured and recorded* total resistance

Measured Total Resistance (Ω)
8.98E+03

12. *Compared measured with expected*

Expected Total Resistance (Ω)	Measured Total Resistance (Ω)	% Error
8.92E+03	8.98E+03	-0.7%

13. *Calculated and recorded* total circuit current

	Expected Current (Amp)
R1	1.12E-03
R6	1.12E-03
Branch 1	696.27E-06

Branch 2 424.99E-06


14. *Measured and recorded* total circuit current

	Measured Current (Amp)
R1	1.10E-03
R6	1.10E-03
Branch 1	679.00E-06
Branch 2	418.00E-06

15. *Compared measured total with expected total*

	Expected Current (Amp)	Measured Current (Amp)	% Error
R1	1.12E-03	1.10E-03	1.9%
R6	1.12E-03	1.10E-03	1.9%
Branch 1	696.27E-06	679.00E-06	2.5%
Branch 2	424.99E-06	418.00E-06	1.6%

16. *Drew a circuit reduction schematic*

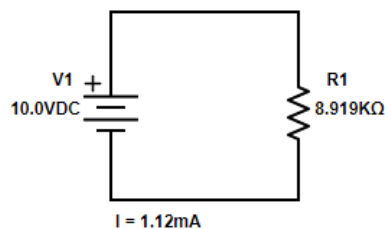

Circuit 3

17. Built Circuit 3 with R_2 equal to 1000Ω. *Note*; zener diodes are operated in reverse bias, with the cathode facing the positive supply.

18. *Measured and recorded* V_{R1} , V_{R2} , V_{ZD} . Recorded findings in the table below.

19. *Calculated and record* I_T , I_{ZD} , and I_{R2} . *Note*: Zener diodes are active components and do not comply with Ohm's Law. To determine I_{ZD} , use Ohm's Law to calculate I_{R1} and I_{R2} then subtract I_{R2} from I_{R1} .

20. Changed R_2 to 470 Ohm

21. *Measured and recorded* V_{R1} , V_{R2} , V_{ZD} . Recorded findings in the table below.

22. **Calculate and record** I_T , I_{ZD} , and I_{R2} . **Note**; The voltage drop across the Zener diode is largely unaffected changes in current through the diode. Zener diodes find application as constant voltage sources.

Voltage Performance		% Voltage Change	% Current Change	Current Performance		Ω
Ω	1000			1000	470	
V_{R1}	7.03E+00	7.10E+00	1.00%	23.43E-03	23.67E-03	I_{R1}
V_{R2}	4.97E+00	4.89E+00	1.61%	4.97E-03	10.40E-03	I_{R2}
V_{ZD}	4.97E+00	4.89E+00	1.61%	18.46E-03	13.26E-03	I_{ZD}
V_T	12.00E+00	11.99E+00		23.43E-03	23.67E-03	$I_{R2} + I_{R1}$

Formulas

Ohm's Law

$$E = IR, I = \frac{E}{R}, R = \frac{E}{I}$$

Where;

E = voltage (Volts)

I = current (Amperes)

R = circuit resistance (Ohms)

% Error

$$\% Error = \frac{\text{measured} - \text{expected}}{\text{expected}} \times 100\%$$

Where;

%Error = % change between measured and expected values

measured = a value taken from direct measurement

expected = a value taken from component or process specifications

Parallel Resistance – Conductance Method

$$R_{equiv} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_n}}$$

Where;

R_{equiv} = circuit total resistance

R = resistance

1/R = conductance in mho's

Parallel Resistance – Product over Sum Method

$$R_{equiv} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Note; Product Over Sum may only be used when there are only 2 parallel loads.

Parallel Resistance – Equal Value Resistance

$$R_{equiv} = \frac{R_{all}}{n}$$

Note; Equal Value Resistance may only be used when there are identical resistance paths through *n* parallel loads.

Circuit 3 Calculations

$$I_{R1} = \frac{V_{R1}}{R_1}$$

$$I_{R2} = \frac{V_{R2}}{R_2}$$

$$I_{ZD} = I_{R1} - I_{R2}$$

$$I_T = I_{R1}$$

Where;

I_{R1} = resistor 1 current

V_{R1} = resistor 1 voltage drop

R₁ = resistor 1 value

I_{R2} = resistor 2 current

V_{R2} = resistor 2 value

R₂ = resistor 2 value (1000 & 470Ω)

I_{ZD} = zener current

I_T = total circuit current

Questions / Conclusions

1. What are the primary characteristics of a combination series / parallel circuit?

Any circuit having both series and parallel connected components is considered a combination series / parallel circuit. The series components of the circuit will have common current paths and the parallel components will have a common voltage supply.

2. Describe the procedure used for circuit reduction analysis for series / parallel circuits?

Procedures for circuit reduction include first combining parallel branch resistance portions into series equivalents and then adding all series components into a total representative resistance component.

3. Using your measured values from Circuit 1, show calculations that demonstrate that Ohm's Law and Kirchhoff's Current Law provide equivalent results. (total current is equal to the sum of the branches)

R1 shows the current through the circuit relative to the source and through R1 and returning from the parallel portion. The voltage source is 10v, the total resistance measured is 2.16k Ω . As $I = V/R$, $I = 10V / 2.16 \text{ k}\Omega = 4.64\text{mA}$

The sum of the currents through branch 1, and branch 2 are:

$$2.61\text{mA} + 1.99\text{mA} = 4.60\text{mA}$$

$$4.64\text{mA} \approx 4.60\text{mA}$$

4. In circuit 3, why did the voltage drop remain relatively constant across R2 with different value resistors? Was Ohm's Law violated?

The stable voltage drop phenomenon seen in circuit 3 is due to the behavior of the 1N4733A Zener diode that was used. When a certain voltage is present at the diode, it will start conducting. This particular diode according to the datasheet has a voltage range up to 5.1V. When the resistor was changed to the 470 Ω resistor, in parallel with the diode, the same voltage was required to be dissipated at the bottom of the circuit. The diode and the 470 Ω resistor, in parallel had the same voltage drop, but the current doubled through the 470 Ω resistor and decreased by approximately 5mA through the diode. Ohm's law wasn't violated, the diode resistance automatically changed from approximately 269 Ω to approximately 369 Ω

Appendix A –Lab Notes

SIERRA COLLEGE	MECH 10 - Lab 08 Series / Parallel Circuits	Mechatronics <i>Real Skills Real Jobs</i>
Name <i>Cape James</i>		<i>9/29/19</i>

Learning Objectives

- Build series / parallel circuits as per a schematic diagram
- Measure electrical values using a digital voltmeter
- Use Ohm's Law to reduce a series /parallel circuit to the simplest form
- Use a data table and schematic diagrams to capture field measurements

Notes:

1. Take all voltage measurements relative to ground (unless otherwise stated)
2. Record relevant measurements and calculation results in data tables
3. Record all measured values on the circuit schematics
4. Use all available precision in calculations, round off answers to 3 significant figures

Materials

Quantity	Description
1	Global Specialties Circuit Trainer
1	Digital multimeter (DMM)
Circuit 1 & 2	
1	R1, R2, R3, R4, R5, R6 – choose any resistors between 1K Ω and 5.6K Ω , each of different value
Circuit 3	
1	Zener diode, 1N4733A, 5.1V
1	R1 – 300 Ω
1	R2 – 470 Ω and 1k Ω

Procedure – Series / Parallel Circuits

Circuit 1

1. Select resistors for circuit 1, 2 and 3 according to the materials chart above. Create a data table that shows;
 - a. Expected resistance values (from resistor color codes); use these values for *all expected value calculations*
2. Build Circuit 1 *without the voltage source connected* (i.e. leave the circuit power supply leads disconnected)
3. **Total Resistance (expected)** - Calculate and record R_T , the total circuit resistance using circuit reduction, expected resistor values and one of the R_{equiv} formulas.
4. **Total Resistance (measured)** – Measure and record R_T and compare the measured value to the expected value using the % Error formula.

5. Set the trainer power supply to 10V. Measure and record V_S , the power supply voltage to three significant figures.
6. **Circuit Currents (expected)** - Calculate and record $I_T = I_{R1}, I_{R2}, I_{R3}$ - expected circuit currents using Ohm's Law, V_S , and R_{Texp} values. Show that total current equals the sum of the branch currents.
7. **Circuit Currents (measured)** Measure and record $I_T = I_{R1}, I_{R2}, I_{R3}$, circuit current using the DMM as an ammeter. Record the values and compare to expected values using the % Error formula.
8. **Reduction schematic** - draw the circuit reduction steps for Circuit 1 on the Circuit Reduction Worksheet

Circuit 2

9. Build circuit 2.
10. Calculate and record total resistance
11. Measure and record total resistance
12. Compare measured with expected
13. Calculate and record total circuit current
14. Measure and record total circuit current
15. Compare measured total with expected total
16. Draw a circuit reduction schematic

Circuit 3

17. Build Circuit 3. *Note*; zener diodes are operated in reverse bias, with the cathode facing the positive supply. $R_2 = 470$
18. Measure and record V_{R1}, V_{R2}, V_{ZD} . Record your findings
19. Calculate and record I_T, I_{ZD} , and I_{R2} . *Note*: Zener diodes are active components and do not comply with Ohm's Law. To determine I_{ZD} , Calculate I_{R1} and I_{R2} then subtract I_{R2} from I_{R1} .
20. Change R_2 to 470 Ohm
21. Measure and record V_{R1}, V_{R2}, V_{ZD} . Record your findings
22. Calculate and record I_T, I_{ZD} , and I_{R2} . *Note*: The voltage drop across the Zener diode is largely unaffected by the change in the load resistor I_{R2} . Zener diodes find application as constant voltage sources.

Formulas

Ohm's Law

$$E = IR, I = \frac{E}{R}, R = \frac{E}{I}$$

Where;

E = voltage (Volts)

I = current (Amperes)

R = circuit resistance (Ohms)

% Error

$$\%Error = \frac{\text{measured} - \text{expected}}{\text{expected}} \times 100\%$$

Where;

$\%Error$ = % change between measured and expected values

measured = a value taken from direct measurement

expected = a value taken from component or process specifications

Parallel Resistance – Conductance Method

$$R_{equiv} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_n}}$$

Where;

R_{equiv} = circuit total resistance

R = resistance

$1/R$ = conductance in mho's

Parallel Resistance – Product over Sum Method

$$R_{equiv} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Note; Product Over Sum may only be used when there are only 2 parallel loads.

Parallel Resistance – Equal Value Resistance

$$R_{equiv} = \frac{R_{all}}{n}$$

Note; Equal Value Resistance may only be used when there are identical resistance paths through n parallel loads.

Circuit 3 Calculations

$$I_{R1} = \frac{(V_S - V_{ZD})}{R_1}$$

$$I_{R2} = \frac{V_{ZD}}{R_2}$$

$$I_{ZD} = I_{R1} - I_{R2}$$

$$I_T = I_{R1}$$

Where;

I_{R1} = resistor 1 current

V_S = source voltage

V_{ZD} = zener voltage

I_{R2} = resistor 2 current

I_{ZD} = Zener diode current

I_T = total circuit current

Questions / Conclusions

1. What are the primary characteristics of a combination series / parallel circuit?
2. Describe the procedure used for circuit reduction analysis for series / parallel circuits?
3. Using your measured values from Circuit 1, show calculations that demonstrate that Ohm's Law and Kirchhoff's Current Law provide equivalent results. (total current is equal to the sum of the branches)

Series / Parallel Circuits

A series parallel circuit has both single and multiple current paths. Some loads are wired in series with the power supply and other loads are wired in parallel, making circuit analysis more complex than simple series or parallel circuits. The current that travels through the circuit is controlled by the applied voltage, series resistance, and branch resistances with the total current flow found using circuit reduction to an equivalent resistance. Total circuit current is found by dividing source voltage by the circuit equivalent resistance.

Kirchoff's Current Law applies, with total circuit current equal to the sum of the branch currents.

$$I_T = \frac{V_S}{R_{equiv}} = I_{B1} + I_{B2} + \dots + I_N$$

Where;

- I_T = total circuit current
- V_S = source voltage
- R_{equiv} = circuit equivalent resistance
- I_{B1} = branch 1 current
- I_{B2} = branch 2 current
- I_{Bn} = branch n current

Parallel Equivalent Resistance

$$R_{equiv} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


General Form

$$R_{equiv} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Two-branch circuits

$$R_T = \frac{R_{all}}{N}$$

Equivalent branch resistances

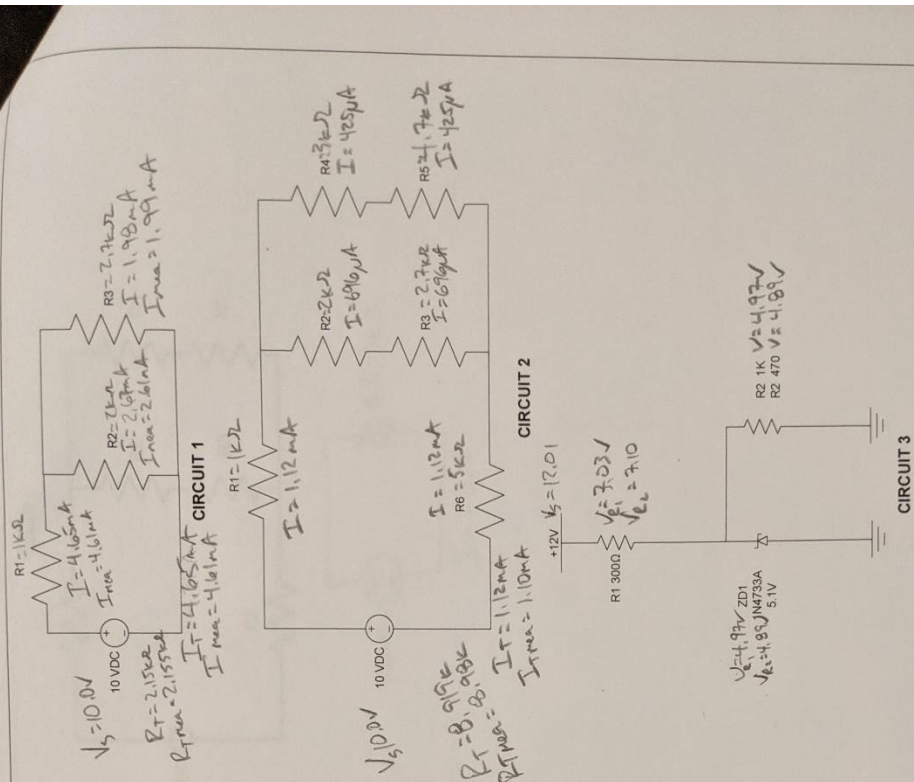

SIERRA COLLEGE		MECH 10 – FUNDAMENTALS OF ELECTRONICS	
Mechatronics		LAB 08 – COMBINATION CIRCUITS	
SIZE	FSCM NO	DWG NO	REV
		MECH10-08	0
SCALE	NONE	SHEET	1 OF 5
DRAWN BY – S GILLETTE			
FEB 2012			

Circuit 1

10 VDC

$R_T = 2.15k\Omega$

$I = 4.65mA$

Circuit 2

10 VDC

$8.91k\Omega$

$I = 1.12mA$

SIERRA COLLEGE

Mechatronics

Real Skills Real Jobs

MECH 10 – FUNDAMENTALS OF ELECTRONICS			
SERIES / PARALLEL CIRCUIT ANALYSIS CIRCUIT REDUCTION WORKSHEET			
SIZE	FSCM NO	DWG NO MECH10-08.3	REV 0
DRAWN BY – SDG		SEPT 2011	
SCALE		SHEET	
NONE		2 OF 5	

Grading Criteria

		Points Possible	Points Earned
Documentation	Abstract, introduction, experiment, data results, conclusions, attachments, clarity, spelling, grammar	10	
Circuit 1	Expected and measured resistance, and current recorded in data table with percent error, circuit reduction diagram complete & accurate	10	
Circuit 2	Expected and measured resistance and, current recorded in data table with percent error, circuit reduction diagram complete & accurate	10	
Circuit 3	Voltages measured, currents calculated for both R_2 values.	10	
Critical Thinking	Questions answered completely & accurately. State conclusions drawn and lessons learned from the lab	10	
On-time submittal	Lab report is submitted in accordance with the assignment due date as posted on Canvas	5	
	Total	55	

Lab Report Format

Abstract - a summary and high-level overview of the lab and its results

Introduction - State the objectives of the laboratory and list the equipment required

Experiment - Describe the procedure used to carry out the lab

Results Data - list data taken in table or graphical format where appropriate

Critical Thinking - State the conclusions drawn and lessons learned from the laboratory activities. Answer any questions found within the lab procedure.

Attachments – grading criteria, verification signatures, circuit diagrams, lab procedures & notes