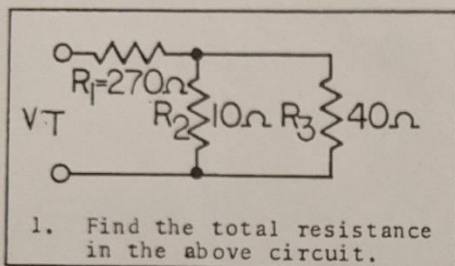


Cayce Beames
 Sept 29, 2019
 MECH-0010
 Professor Gillette

WORKSHEET

COMBINATION CIRCUIT ANALYSIS

Solve the following circuit problems. Be certain to show work and record your answer in the answer box.



Show work


$$R_T = R_1 + \left(\frac{R_2 \times R_3}{R_2 + R_3} \right)$$

$$= 270\Omega + \left(\frac{40\Omega}{50} \right)$$

$$= 270\Omega + 8\Omega$$

$$= 278\Omega$$

1. 278Ω

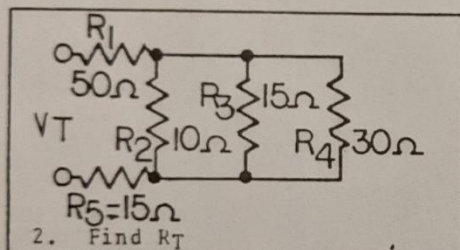

Show work

$$R_T = 50\Omega + \left(\frac{1}{\frac{1}{10} + \frac{1}{15} + \frac{1}{30}} \right) + 15\Omega$$

$$= 50 + \left(\frac{1}{\frac{2}{30} + \frac{2}{30} + \frac{1}{30}} \right) + 15\Omega$$

$$= 50 + \left(\frac{1}{\frac{5}{30}} \right) + 15$$

$$= 50 + 6 + 15$$

$$= 71\Omega$$

2. 70Ω


- 3A. Draw a combination circuit which contains the following resistors; a 39 ohm and 27 ohm connected in series with two parallel resistors each having a value of 33 ohms.
- 3B. Find the total resistance of the circuit.

Show work


$$R_T = 39 + 27 + \left(\frac{33}{2} \right)$$

$$= 66 + 16.5$$

$$= 82.5\Omega$$

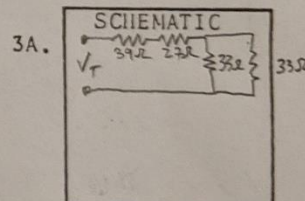

3B. 82.5Ω

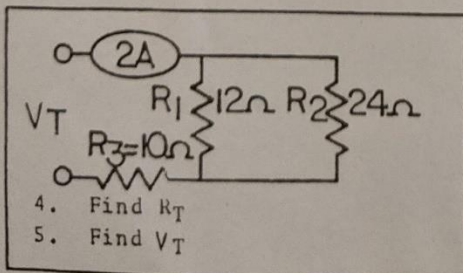

Show work

$$R_T = 10 + \left(\frac{12 \times 24}{12 + 24} \right)$$

$$= 10 + \left(\frac{288}{36} \right)$$

$$= 10 + 8$$

$$= 18\Omega$$


$$V_T = 2A \times 18\Omega$$

$$= 36V$$

4. 18Ω

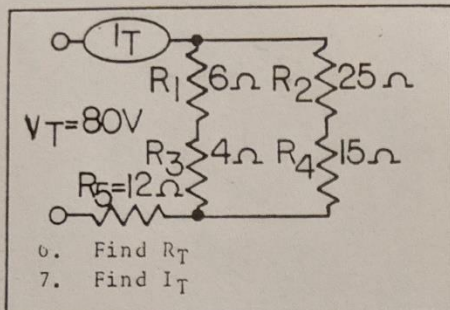5. 36V

Cayce Beames
 Sept 29, 2019
 MECH - 0010
 Professor Gillette



Show work

$$R_T = \frac{(6+4) \times (25+15)}{(6+4) + (25+15)} + 12$$

$$= \frac{10 \times 40}{30} + 12$$


$$= \frac{400}{30} + 12$$

$$= 13 + 12 = 25\Omega$$

$$I_T = \frac{80V}{25\Omega} = 3.2A$$

6.

7.

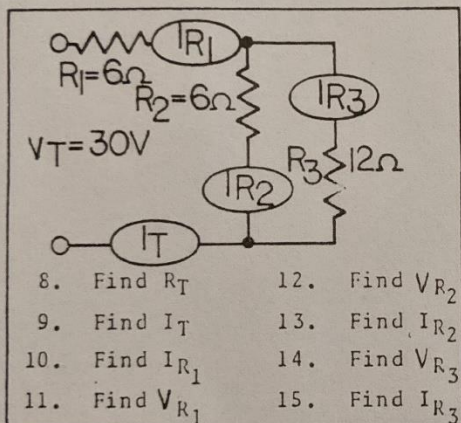

Show work

$$R_T = 6 + \frac{6 \times 12}{6 + 12}$$

$$= 6 + \frac{72}{18}$$

$$= 6 + 4 = 10\Omega$$

$$I_T = \frac{30V}{10\Omega} = 3A$$

$$I_{R1} = 3A$$

$$V_{R1} = 3A \times 6\Omega = 18V$$

$$V_{R2} = 30V - 18V = 12V$$

$$I_{R2} = \frac{12V}{6\Omega} = 2A$$

$$V_{R3} = 30V - 18V = 12V$$

$$I_{R3} = \frac{12V}{12\Omega} = 1A$$

8.

9.

10.


11.

12.

13.

14.

15.

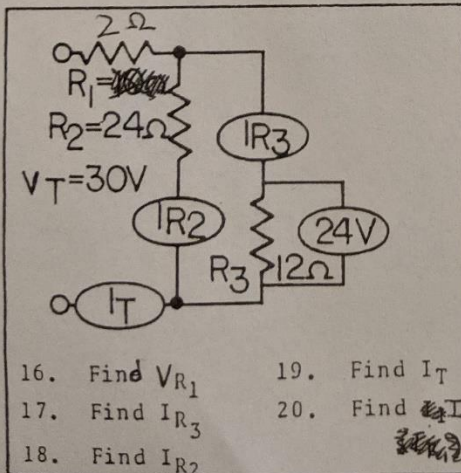

Show work

$$V_{R1} = 30V - 24V = 6V$$

$$I_{R3} = \frac{24V}{12\Omega} = 2A$$

$$I_{R2} = \frac{24V}{24\Omega} = 1A$$

$$I_T = 2A + 1A = 3A$$

$$I_{R1} = \frac{6V}{2\Omega} = 3A$$

16.

17.


18.

19.

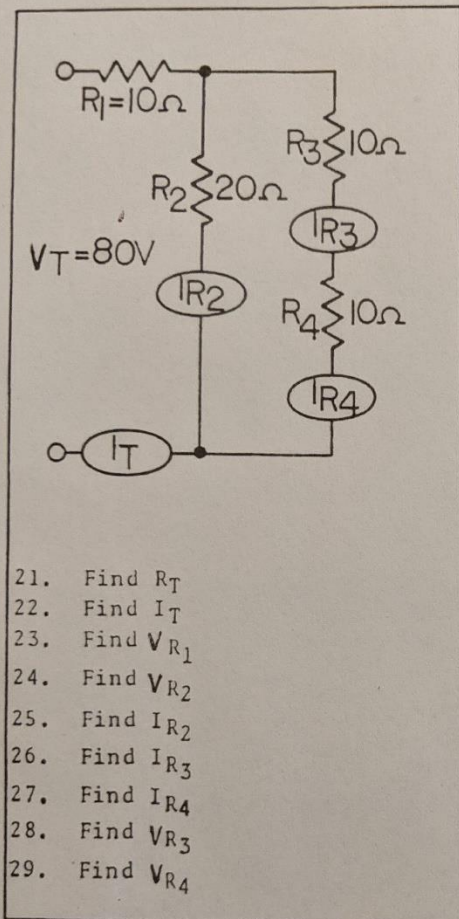20.

Pg 2013

Cayce Beames
 Sept 29, 2019
 MEZH-0010
 Professor Grillette



Show work
 $R_T = 10 + \frac{(20 \times (10+10))}{20+(10+10)}$
 $= 10 + \frac{(20 \times 20)}{20+20}$
 $= 10 + \frac{400}{40}$
 $= 10 + 10 = 20\Omega$
 $I_T = \frac{80V}{20\Omega} = 4A$
 $V_{R1} = 4A \cdot 10\Omega = 40V$
 $V_{R2} = 80V - 40V = 40V$
 $I_{R2} = \frac{40V}{20\Omega} = 2A$
 $I_{R3} = \frac{40V}{20\Omega} = 2A$
 $I_{R4} = \frac{40V}{20\Omega} = 2A$
 $V_{R3} = 2A \cdot 10\Omega = 20V$
 $V_{R4} = 2A \cdot 10\Omega = 20V$

21. 20Ω
 22. $4A$
 23. $40V$
 24. $40V$
 25. $2A$
 26. $2A$
 27. $2A$
 28. $20V$
 29. $20V$