

SCORE:

GRADE:

Name: Cayce Beames

Date: 9/11/19

Period:

WORKSHEET

OHM'S LAW

1. OHM'S law states that current is directly proportional to a) voltage and inversely proportional to b) resistance.
2. Using the OHM'S law triangle below, write the 3 OHM'S law formulas.



1A. voltage

1B. resistance

2A.  $V = I \times R$

2B.  $I = V / R$

2C.  $R = V / I$

MATCHING

3. Current is measured in:
4. V is the letter symbol for:
5. R is the letter symbol for:
6. Voltage is measured in:
7. Resistance is measured in:
8. I is the letter symbol for:
9. Conductance is measured in:

- a. resistance
- b. volts
- c. voltage
- d. amperes
- e. current
- f. OHMS
- g. siemens

3. d

4. c

5. a


6. b

7. f

8. e

9. g

10. Using the circuit below:

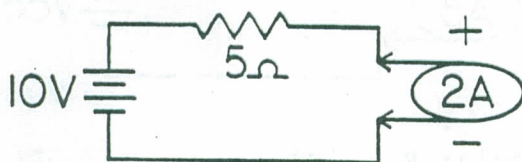

- a. Identify the "R" (resistance) value in the circuit.
- b. Identify the "V" (voltage) value in the circuit.
- c. Identify the "I" (current) value in the circuit.

10A. 5Ω

10B. 10Vdc

10C. 2A

Name: Cayce Beames

Date: 9/11/19

Period:

OHM'S LAW MATCHING:

18.  $V = 52V$ ,  $R = 4\Omega$ ,  $I =$  \_\_\_\_\_

19.  $R = 1,000\Omega$ ,  $I = .2A$ ,  $V =$  \_\_\_\_\_

20.  $I = .5A$ ,  $V = 15V$ ,  $R =$  \_\_\_\_\_

21.  $I = .01A$ ,  $R = 4,700\Omega$ ,  $V =$  \_\_\_\_\_

22.  $V = 15V$ ,  $R = 100\Omega$ ,  $I =$  \_\_\_\_\_

23.  $I = 2A$ ,  $V = 4,560V$ ,  $R =$  \_\_\_\_\_

a.  $.15A$

b.  $13A$

c.  $2280\Omega$

d.  $47V$

e.  $200V$

f.  $30\Omega$

18.

b

19.

e

20.

f

21.

d

22.

a

23.

c

Work for Prob. 18

$$I = 52V / 4\Omega$$

$$I = 13A$$

b.

Work for Prob. 21

$$V = .01A * 4,700\Omega$$

$$V = 47$$

d.

Work for Prob. 19

$$V = 1,000\Omega * .2A$$

$$V = 200A$$

e.

Work for Prob. 22

$$I = 15V / 100\Omega$$

$$I = .15A$$

a.

Work for Prob. 20

$$R = 15V / .5A$$

$$R = 30\Omega$$

f.

Work for Prob. 23

$$R = 4,560V / 2A$$

$$R = 2280\Omega$$

c.