
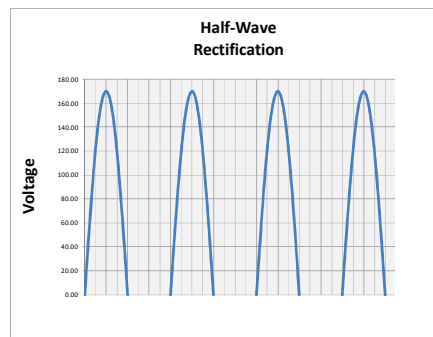


Class 19 DC Power Supplies

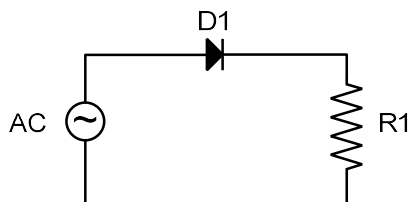



- Rectifiers
 - Half-wave
 - Positive or negative alternations passed




- Rectifiers

- Full Wave

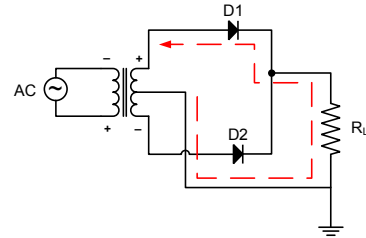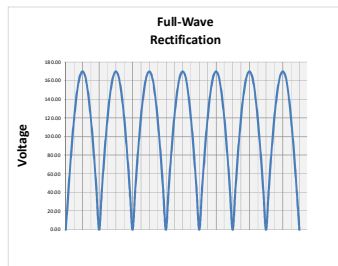- Positive alternations
 - D1 conducts
 - Negative alternations
 - D2 conducts



Positive Alternation


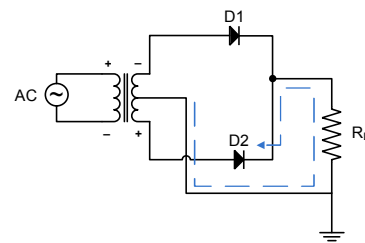


Negative Alternation


- Rectifiers

- Bridge

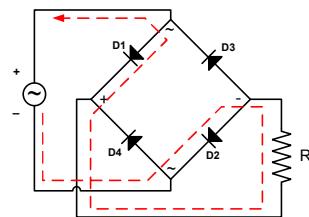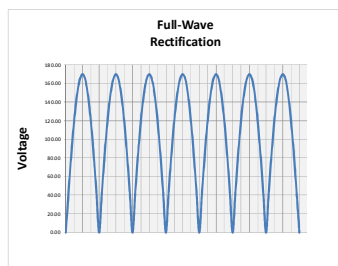- Positive alternations
 - D1 & D2 conduct
 - Negative alternations
 - D3 & D4 conduct




Positive Alternation

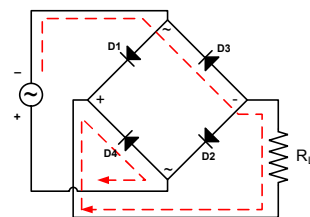

Negative Alternation


- DC Power Supply

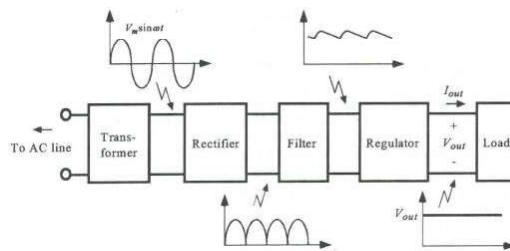- A device that supplies electrical energy as direct current
- Functions
 - Voltage transformation
 - Energy conversion
 - Filtration
 - Regulation
 - Isolation
 - Protection



- DC Power Supply


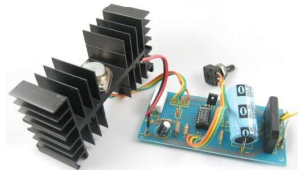
- Types
 - Linear – regulates output using transistors operating in linear mode. Power is supplied as a continuous voltage and current
 - Switched Mode – regulates output using transistors operating in saturation mode. Power is supplied as voltage pulses with controlled duty cycle



- DC Power Supply

- Functions

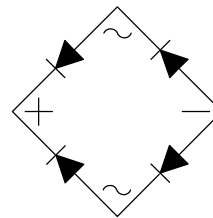
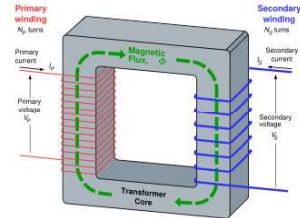
- Voltage transformation – the use of an AC transformer to step down line voltage
 - Energy conversion – the conversion of electrical energy from alternating to direct current



- DC Power Supply

- Functions

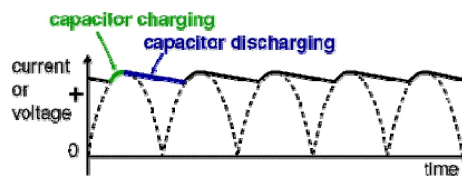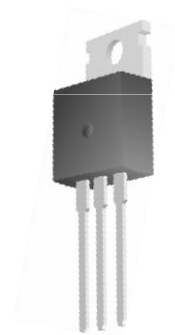
- Filtration – the reduction of pulsating DC ripple
 - Regulation – the control of a power supply's output current, voltage or both



- DC Power Supply

- Functions

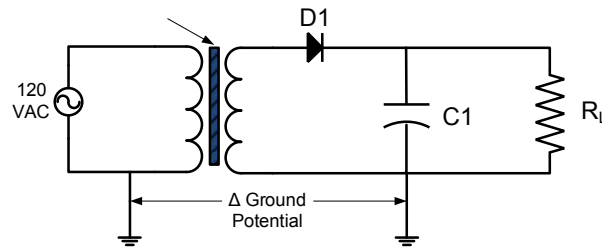- Isolation – the prevention of charge transference between electrical systems.
 - Ground loops - Noise, interference, shock hazard



- DC Power Supply



- Functions

- Protection – the protection of power supply hardware from electrical faults
 - Over Current
 - Over / Under Voltage
 - Over / Under Frequency





Circuit Breaker






Fuse

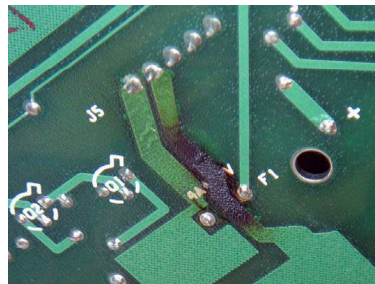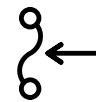

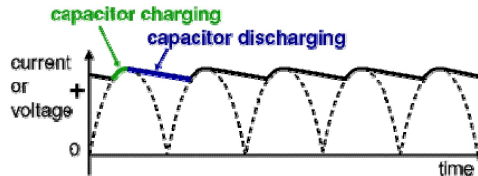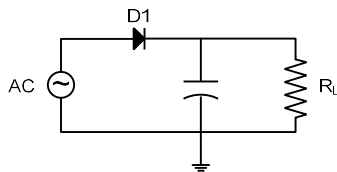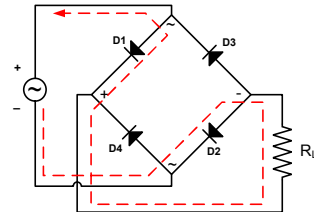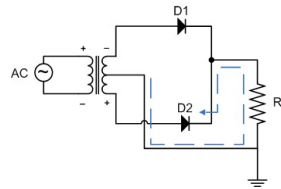- DC Power Supply
 - Linear PS Functions
 - Voltage transformation
 - AC transformer
 - Energy conversion
 - AC to DC
 - Filtration
 - Capacitor




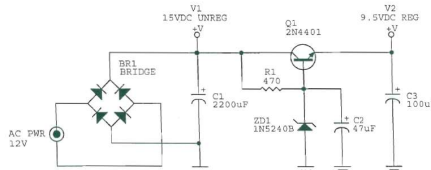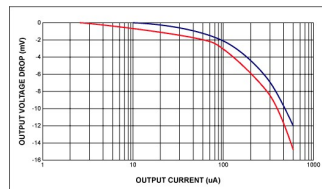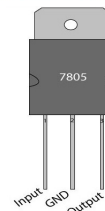- DC Power Supply
 - Linear PS Functions
 - Regulation – constant output voltage
 - **Load regulation** – the change in output voltage caused by a load change
 - e.g. 100mV @ 1 amp
 - **Line regulation** – the change in output voltage caused by a change input voltage
 - e.g. 130mV / 1 volt




- DC Power Supply
 - Switched Mode PS Functions

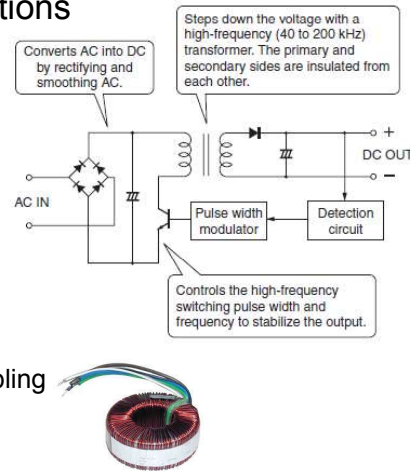- Energy Conversion
 - Rectifier
- Filtration
 - Capacitors
- Voltage transformation
 - Primary – PWM
 - Secondary – filtered DC
- Isolation
 - Transformer magnetic coupling



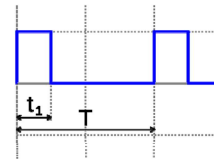- DC Power Supply
 - Switched Mode PS Functions
 - Pulse width modulation



Duty Cycle

$$V_{eff} = D \times V_{MAX} + (1 - D) \times V_{min}$$

Where;

D = duty cycle (%)

 V_{MAX} = max voltage V_{MIN} = min voltage

D: 0%

- DC Power Supply
 - Linear v Switched

	Linear PS	SMPS
Size & Weight	Xfmr & heat sinks add bulk & size	Smaller & lighter (HF inductor v xfmr, heat sinks)
Efficiency	30 to 40% (function of V_{in} versus V_{out})	60 to 90% (low resistive losses between input & output, precise load regulation)
Radio Frequency Interference	Mild high frequency from AC rectifier	Strong due to current switching

- Lab 19 – MagLev Power Supply

Learning Objectives

- Measure the output of a bridge rectifier
- Measure ripple voltage from a DC power supply
- Visualize voltage ripple in a DC power supply output.
- Understand the benefits of filtered and regulated power supplies

		Points Possible
Documentation	Quality of documentation (neatness, clarity, spelling, grammar), Expected and measured values recorded on schematic diagram	10
Setup	Power supply voltages measured and calculated	5
Unfiltered Bridge Rectifier	Waveform captured, frequency calculated,	5
Filtered Bridge Rectifier	LED V_F , C1 voltage drop, V_{PP} , V_{R2} , I_{R2} , Q1 V_{PP} , ripple waveform captured	10
Conclusions	Questions answered completely & accurately.	20
	Total	50