

# Quiz 02 - Series Parallel Circuits, Batteries

**Due** Dec 14 at 11:59pm**Points** 155**Questions** 30**Available** Aug 24 at 12pm - Dec 14 at 11:59pm 4 months**Time Limit** None**Allowed Attempts** 2

## Instructions

Covers lab and lecture topics from classes 6 through 9

Do not include include units of measure in your calculated numeric answers

## Attempt History

	Attempt	Time	Score
KEPT	<a href="#">Attempt 2</a>	7 minutes	150 out of 155
LATEST	<a href="#">Attempt 2</a>	7 minutes	150 out of 155
	<a href="#">Attempt 1</a>	53 minutes	145 out of 155

Score for this attempt: **150** out of 155

Submitted Oct 8 at 8:56pm

This attempt took 7 minutes.

### Question 1

**0 / 5 pts**

Select two answers that apply

Series circuits are characterized by;

- ☒ a single applied voltage
- ☒ equal current in all parts of the circuit
- ☐ a single current path
- ☐ multiple current paths

You Answered

Correct!

Correct Answer

**Question 2****5 / 5 pts**

In a series circuit, total resistance is equal to

- ☐ the double inverse of the series resistance sum
- ☒ the sum of all series connected resistance
- ☐ the RMS resistance value
- ☐ the product over sum of the series resistance


**Correct!****Question 3****5 / 5 pts**

In a parallel circuit, total resistance is equal to

- ☐ the product over the quotient of the resistances
- ☐ the square root of the series resistance
- ☐ the RMS resistance value
- ☒ the inverse of the conductance sum

**Correct!****Question 4****5 / 5 pts**


Find the total resistance for this circuit.

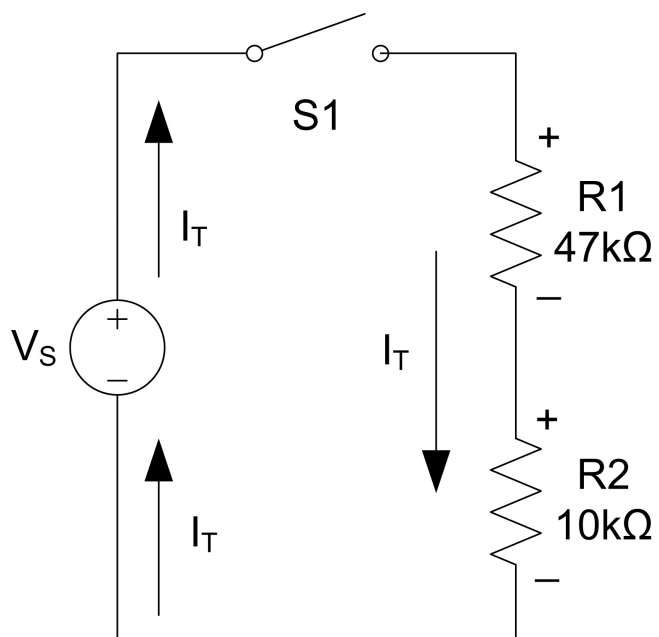**Correct!****correct Answers**


57,000 (with margin: 1,140)

**Question 5****5 / 5 pts**

Find the total resistance for this circuit.

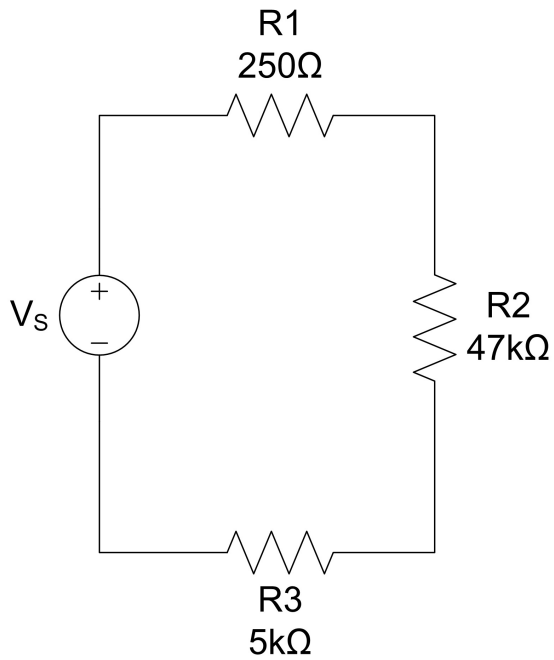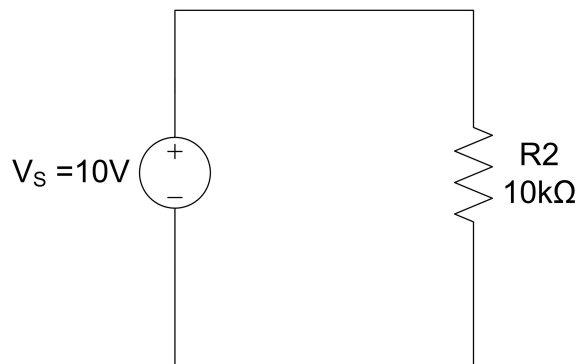
**Correct!****Correct Answers** 52,250 (with margin: 1,045)**Question 6****5 / 5 pts**

Find the total circuit current. Enter your answer in milliamps. Do not include units in your answer.




**Correct!****Correct Answers**

1 (with margin: 0.02)

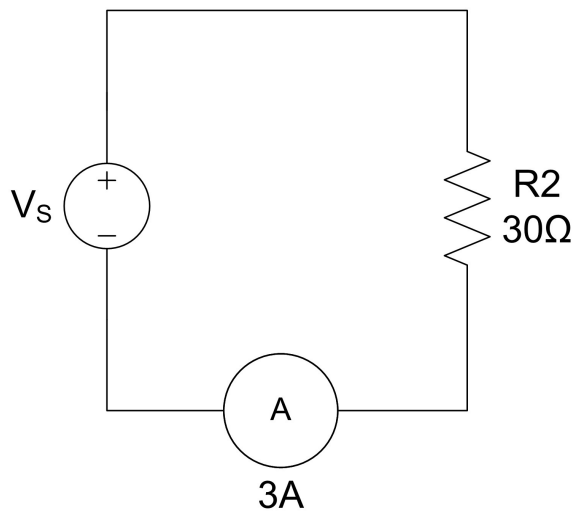**Question 7****5 / 5 pts**Find the circuit source voltage  $V_S$ **Correct!****Correct Answers**

90 (with margin: 1.8)

**Question 8****5 / 5 pts**Find the circuit source voltage  $V_S$

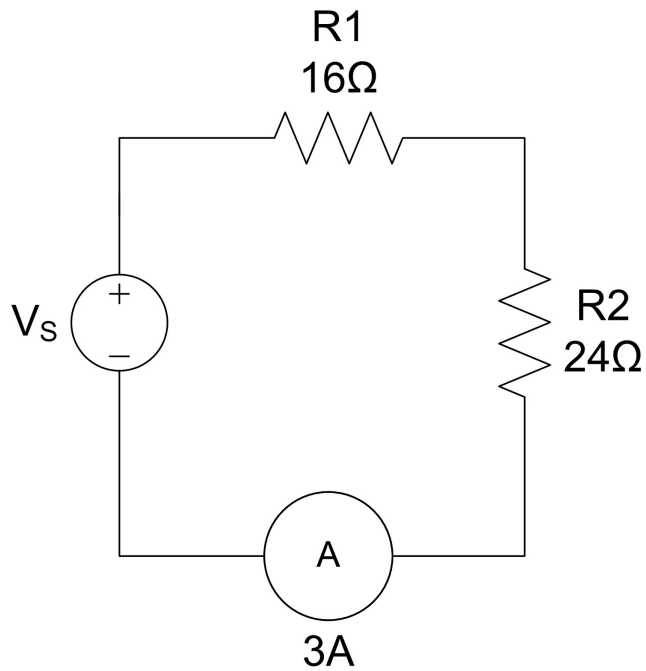**Correct!**

120

**Correct Answers**

120 (with margin: 2.4)

**Question 9****5 / 5 pts**


Total series resistance is directly proportional to

**Correct!**

- ☒ source voltage
- ☐ parallel resistance
- ☐ total current
- ☐ capacitive reactance

**Question 10****5 / 5 pts**

Find the voltage drop across R1

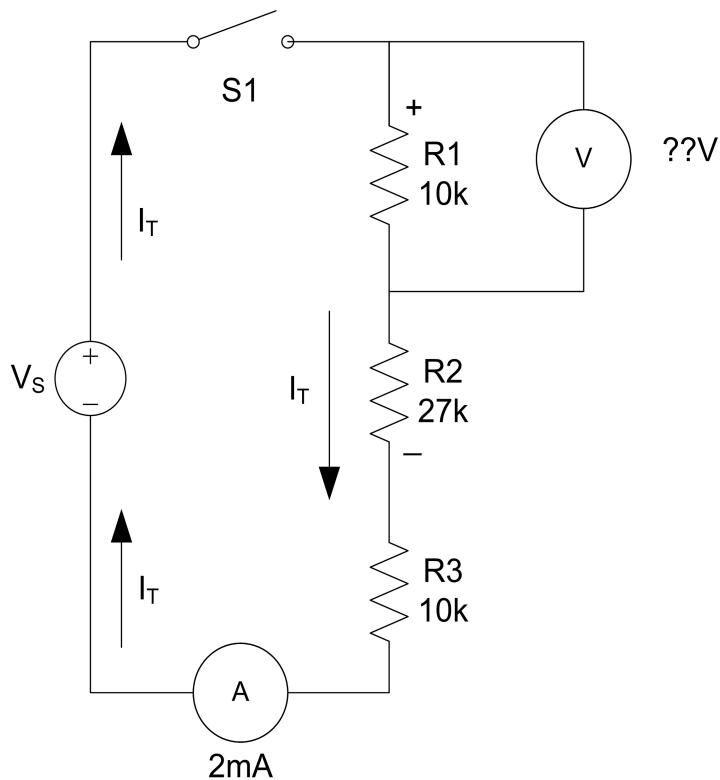

Question 08

Correct!

20


Correct Answers

20 (with margin: 1)

**Question 11**

**5 / 5 pts**

Find the voltage drop across R2

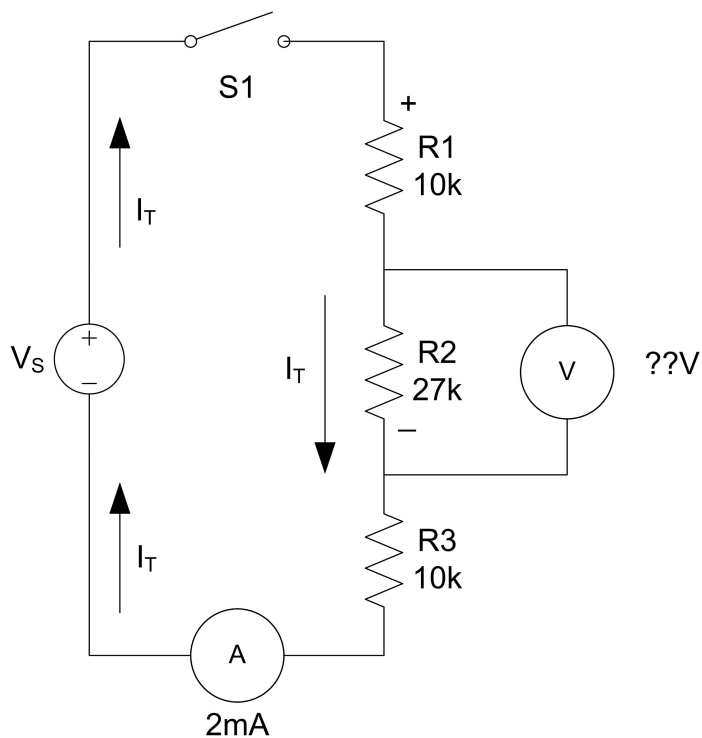**Correct!**


54

**Correct Answers**

54 (with margin: 1.08)

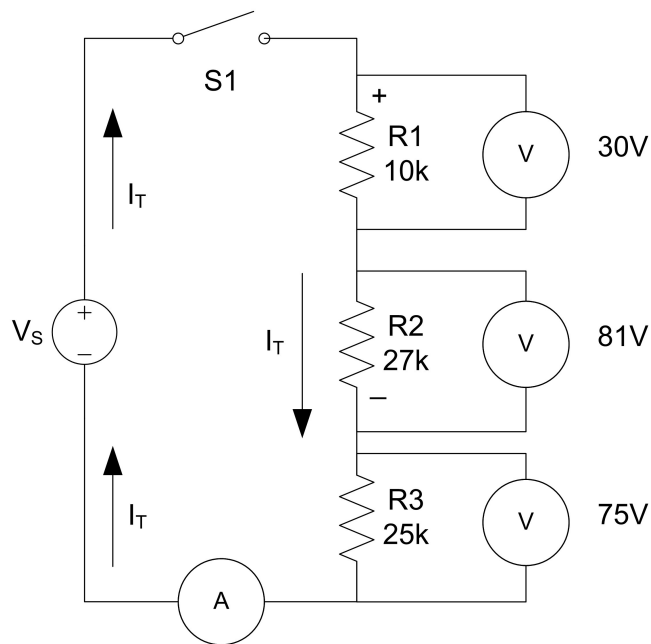**Question 12****5 / 5 pts**Find source voltage  $V_S$



**Correct!**

186

**Correct Answers**

186 (with margin: 3.72)

**Question 13****5 / 5 pts**


Select two answers that apply

Parallel circuits are characterized by;

**Correct!**☒ equal voltage across parallel components☐ different component voltage drops☐ equal current in all parts of the circuit**Correct!**☒ current paths are inversely proportional to resistance

**Question 14****5 / 5 pts**

Find the total circuit resistance

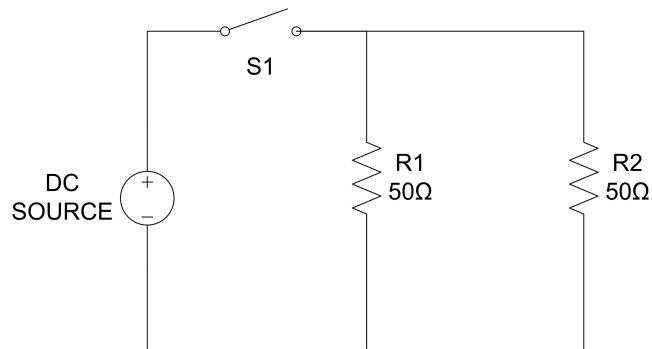**Correct!**


25

**Correct Answers**

25 (with margin: 1.25)

**Question 15****5 / 5 pts**

Find the total circuit resistance

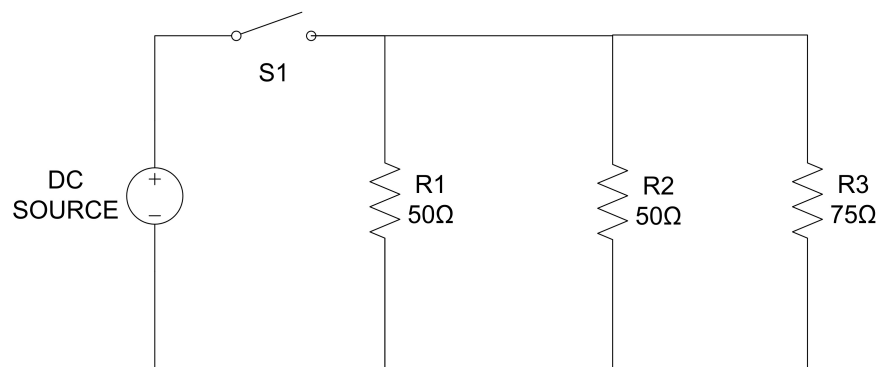

Question 15

**Correct!**


18.75

**Correct Answers**

18.75 (with margin: 0.375)

**Question 16****5 / 5 pts**

Use Ohm's law to find branch current  $I_{R1}$ . Give your answer in milliamps.

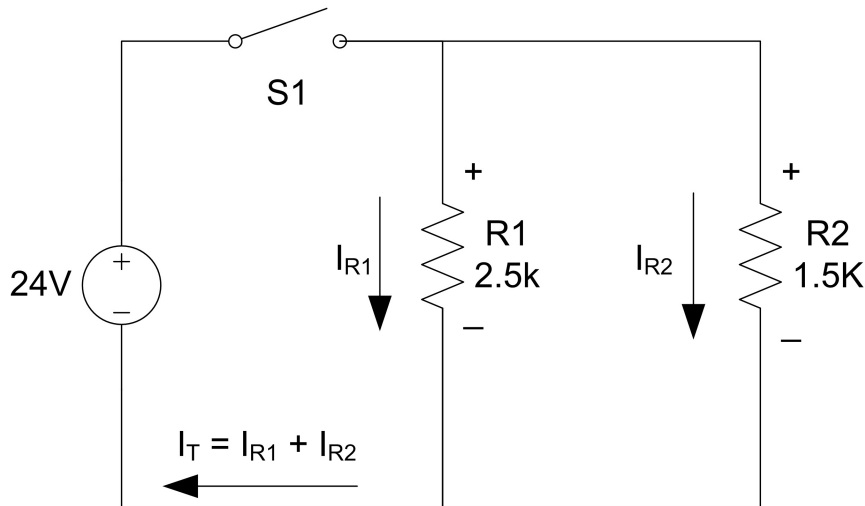**Correct!**


9.6

**Correct Answers**

9.6 (with margin: 0.196)

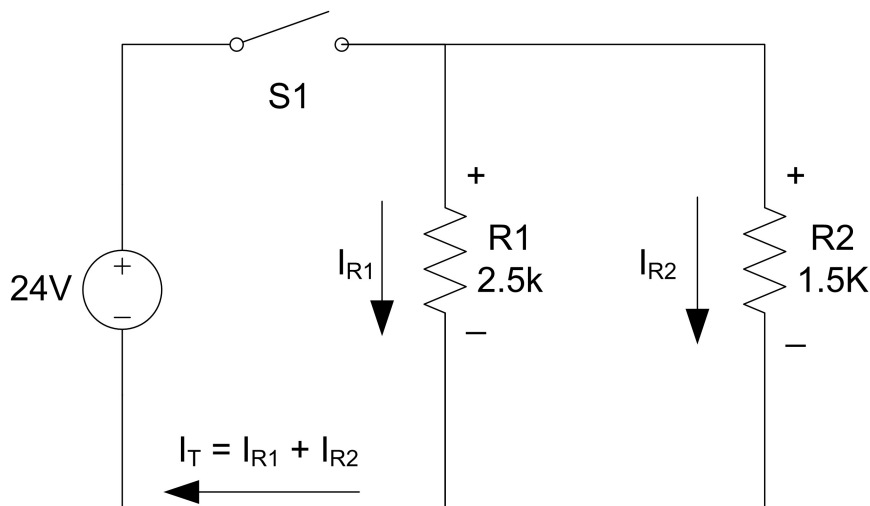**Question 17****5 / 5 pts**

Use Ohm's law to find branch current  $I_{R2}$ . Give your answer in milliamps.



**Correct!**


16

**Correct Answers**

16 (with margin: 0.32)

**Question 18****5 / 5 pts**

Find the total circuit current  $I_T$ . Give your answer in milliamps.

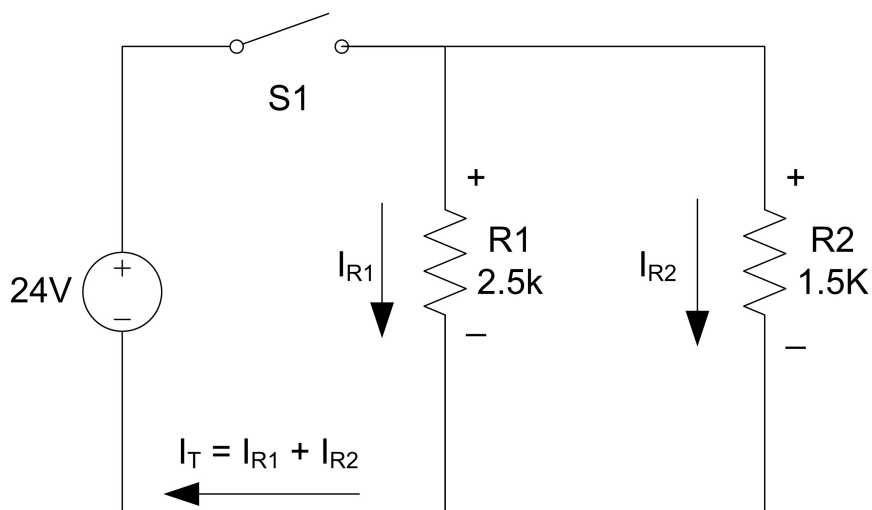**Correct!**


25.6

**Correct Answers**

25.6 (with margin: 0.512)

**Question 19****5 / 5 pts**

Find the total resistance for this circuit. Give your answer in Ohms.

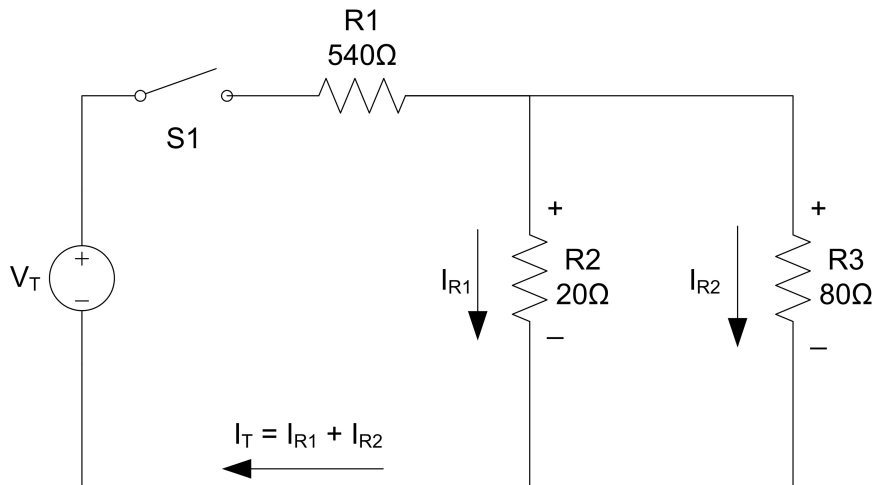**Correct!**


556

**Correct Answers**

556 (with margin: 11.12)

**Question 20****5 / 5 pts**

Find the total current for this circuit using Ohm's Law. Give your answer in milliamps.

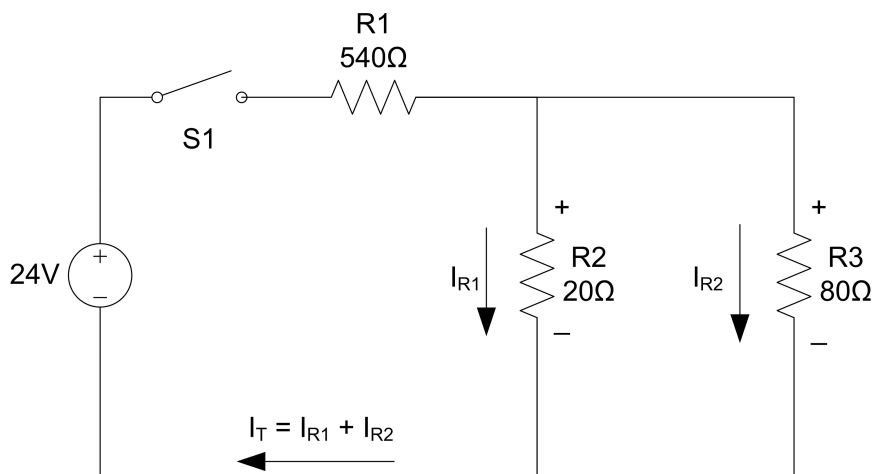**Correct!**

43.165

**Correct Answers**

43.16 (with margin: 0.863)

**Question 21****5 / 5 pts**

Identify two characteristics of a combination series-parallel circuit (check two boxes)

☐ series components are inversely proportional to resistance

**Correct!**

Parallel components may be in parallel with individual or combinations of components


☐ parallel component resistance is additive

**Correct!**

Series components may be in series with individual or combinations of components

**Question 22****5 / 5 pts**

Which three circuit components share a common current path (series connected)?

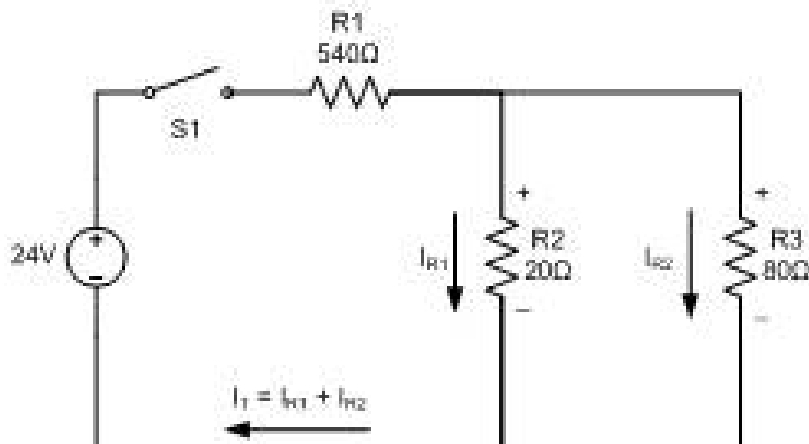
**Correct!**

☒ The voltage source, switch 1, resistor 1

- ☐ Resistor 1, resistor 2, resistor 3
- ☐ Switch 1, resistor 1, resistor 3
- ☐ Resistor 1, resistor 2

**Question 23****5 / 5 pts**


Which circuit components share a common voltage (parallel connected)

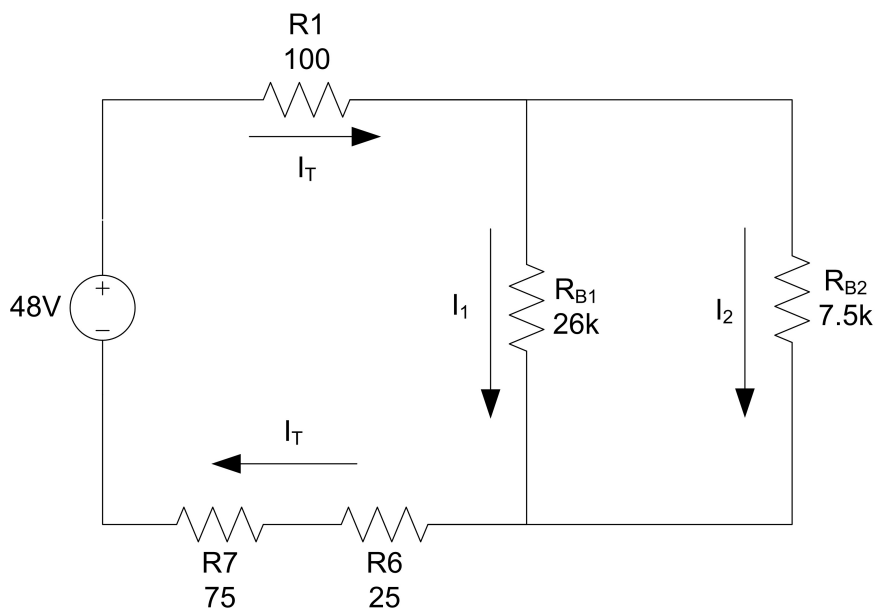**Correct!**

- ☒ The voltage source, RB1, RB2
- ☐ The voltage source, R1, R6, R7
- ☐ R1, RB1, RB2
- ☐ R1, R6, R7

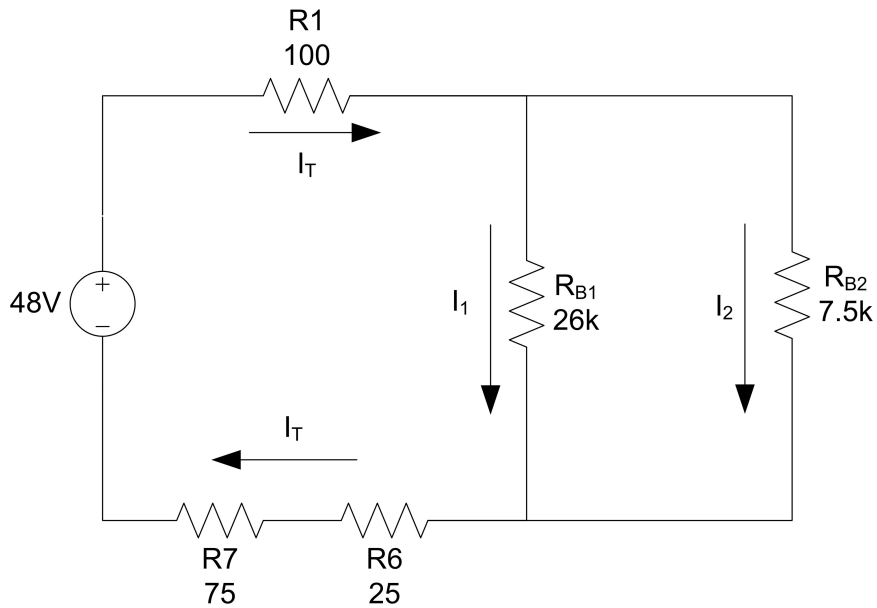**Question 24****5 / 5 pts**

Find the total circuit current. Give your answer in milliamps.



Correct!

7.972

Correct Answers 7.97 (with margin: 0.159)

### Question 25

5 / 5 pts

A battery is

- ☐ An electron centrifugal pump that pumps charge through a circuit
- ☐ A current separation device that divides current into multiple paths
- ☐ The perfect energy storage device

Correct!

- ☒ One or more electro-chemical cells that convert chemical energy into electrical energy



**Question 26****5 / 5 pts**

A primary cell is not rechargeable.

**Correct!**☒ True☐ False**Question 27****10 / 10 pts**

Match the battery characteristic with it's description

**Correct!****Specific energy**

Energy per unit mass ▼

**Correct!****Energy density**

Energy per unit volume ▼

**Correct!****Capacity**

The charge produced at a { ▼

**Correct!****Energy cost**

The cost per unit power ▼

**Question 28****5 / 5 pts**

A battery's capacity rating is 500mAh @ 50mA. What is the current in mA for a 2-C discharge rate?

Give your answer in milliamps.

**Correct!**

100

**Correct Answers**

100 (with margin: 5)

**Question 29****5 / 5 pts**

Battery charge and discharge rates have no effect on battery capacity or performance.

☐ True☒ False**Correct!****Question 30****5 / 5 pts**

Cell internal resistance is increased at high current flows.

☒ True☐ False**Correct!****Quiz Score: 150** out of 155