

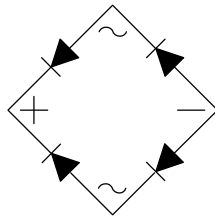
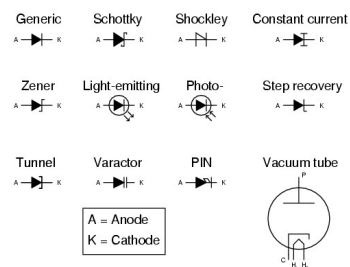
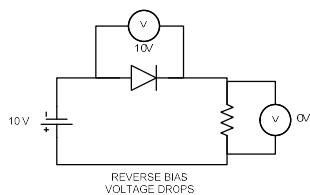
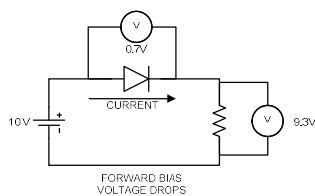


Class 18

Diodes & Rectifiers

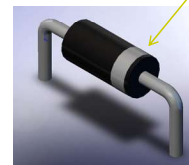


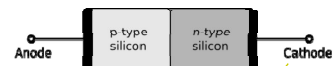
- **Diodes**
 - A two-terminal semiconductor that allows current flow in one direction



- Diodes

- Ratings

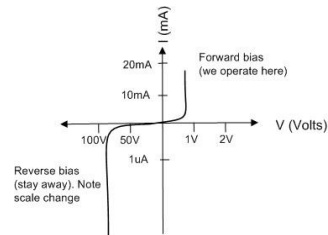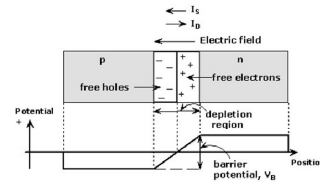- Forward voltage drop** (V_F) – also barrier potential, is the forward conducting junction voltage
 - Silicon – 0.7 V
 - Germanium – 0.3 V
 - Average forward current** – the maximum sustainable forward current
 - Peak reverse voltage** – also breakdown voltage, is the largest sustainable reverse bias voltage



- Diodes

- Rectifier diode

- For AC to DC conversion
 - High forward current
 - Rugged packaging



Type and ordering number	V _{RSM}	V _{RRM}	I _{FAVM}	I _{F3M}		V _{F0}	r _F	T _{VJM}	R _{thJC}	R _{thCH}	F _m
** = V _{RSM} /100 V		T _{VJM}	T _c = 85°C	8.3 ms T _{VJM}	10 ms T _{VJM}	T _{VJM}	T _{VJM}				
	V	V	A	kA		V	mΩ	°C	K/W		kN
5SDD 40B0200	200	200	6130	50.0	45.0	0.80	0.030	170	10	5	22
5SDD 71B0200	200	200	7110	60.0	55.0	0.74	0.026	170	10	5	22

- Diodes

- Switching diode



- High frequency switching
 - Reverse recovery time – time required to switch polarities
 - $< 50\text{nS}$
 - Low current & voltage ratings
 - Applications – communications & computers



- Diodes


- Zener diode

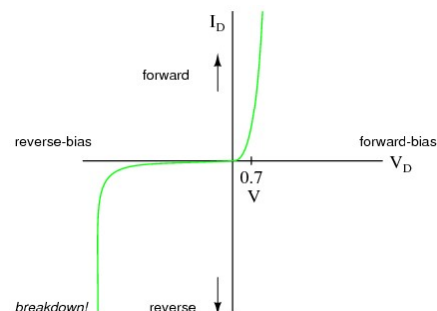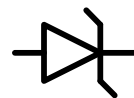- A reverse biased diode that operated at reverse breakdown voltage
 - Designed for specific voltages
 - Voltage regulator
 - Power Rating
 - $P_Z = V_Z \times I_R$
 - Usually in series with load resistor



- Diodes

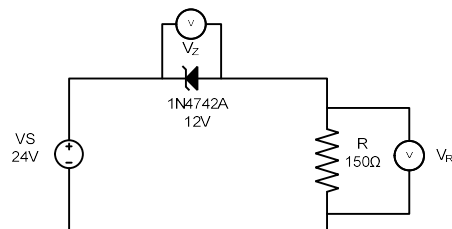- Zener diode
 - Power Rating Circuit Example
 - 1N4742A – 12V @ 1 watt



$$I_R = \frac{(V_S - V_Z)}{R}$$

$$I_R = \frac{(24V - 12V)}{150\Omega}$$

$$I_R = ?$$




$$P_Z = V_Z \times I_R$$

$$P_Z = 12V \times I_R$$

$$P_Z = ?$$

- Diodes

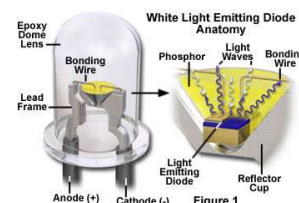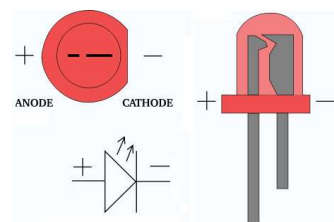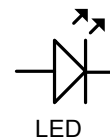
- Light emitting diodes
 - Function
 - Electrons emit photons between conduction & valence band jumps
 - Materials
 - Gallium, arsenic, phosphorous, carbon (colors)
 - Specifications
 - Operate forward biased (1.4 to 2V)
 - 5 to 50mA, series load resistor common




- Diodes

- Photodiodes

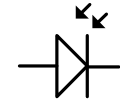- Senses and responds to light intensity
 - Materials
 - Silicon, germanium, indium
 - Operations
 - Photodiode mode
 - Reverse bias
 - Photovoltaic mode
 - Zero bias




Photodiode


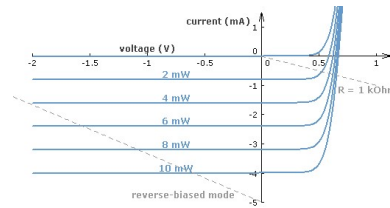


- Rectifiers


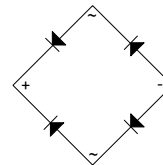
- A diode assembly that converts AC to pulsating DC
 - Types
 - Half-wave
 - Full wave
 - Bridge



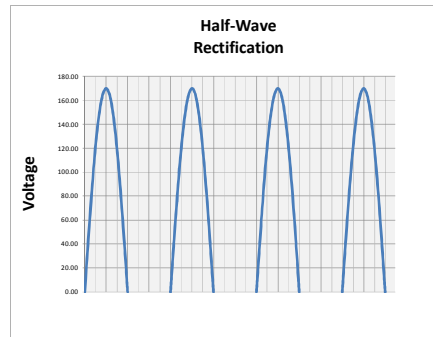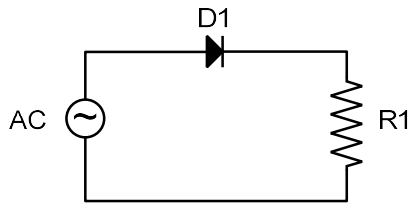
- Rectifiers
 - Half-wave
 - Positive or negative alternations passed



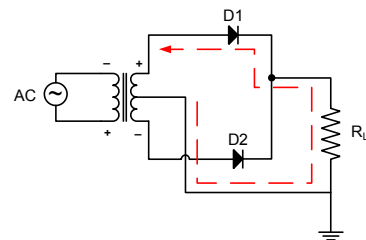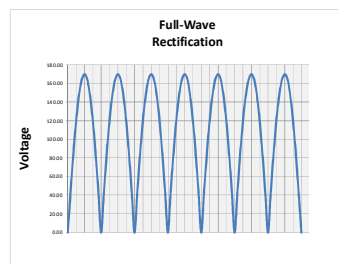- Rectifiers
 - Full Wave
 - Positive alternations
 - D1 conducts
 - Negative alternations
 - D2 conducts



Positive Alternation


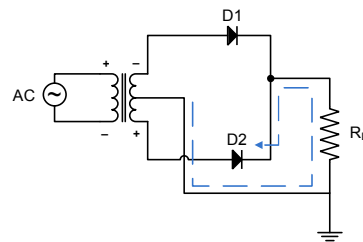


Negative Alternation


- Rectifiers

- Bridge

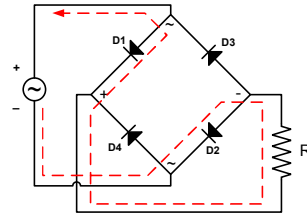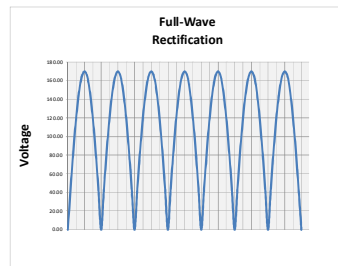- Positive alternations
 - D1 & D2 conducts
 - Negative alternations
 - D3 & D4 conducts



Positive Alternation

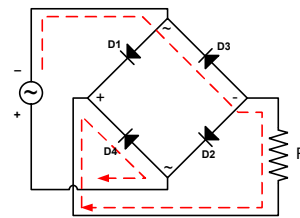


Negative Alternation

- Rectifiers

- Ripple

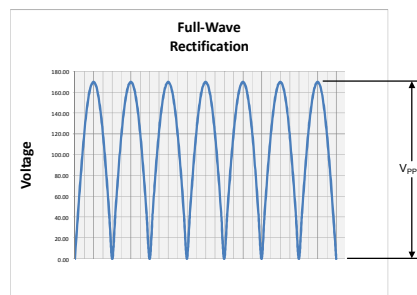- The unwanted periodic variation in the DC output of a rectifier
 - Acts like AC



- Rectifiers

- Ripple

- Capacitive filter



- V_{PP} – ripple voltage

$$V_{PP} = \frac{I}{fC}$$

Half-wave

$$V_{PP} = \frac{I}{2fC}$$

Full-wave

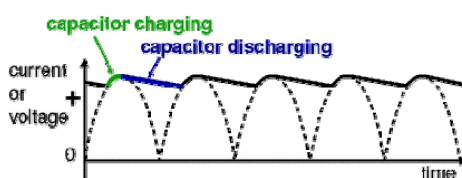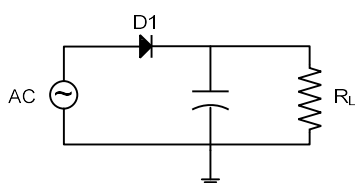

- Lab 18 – Rectifiers

Learning Objectives

- Build and test a half-wave rectifier
- Build and test a full-wave rectifier
- Visualize and analyze rectifier waveforms
- Test a filter capacitor's impact on rectifier waveform

		Points Possible
Documentation	Quality of documentation (neatness, clarity, spelling, grammar), Expected and measured values recorded on schematic diagram	10
Half-wave Rectifier	Diode test results recorded, test point A & B waveforms represented with amplitude & period, frequencies calculated	10
Half-wave Rectifier, Filtered	Rectifier output recorded with DMM & DO-scope, ripple recorded	10
Full-wave Rectifier	Diode test results recorded, test point A & B waveforms represented with amplitude & period, frequencies calculated	10
Full-wave Rectifier, Filtered	Rectifier output recorded with DMM & DO-scope, ripple recorded	10
Conclusions	Questions answered completely & accurately.	20
Total		70