



|   |  |   |
|---|--|---|
|  | MECH 10 - Lab 10<br>Light Activated Switch | <br><i>Real Skills Real Jobs</i> |
| Name: Cayce Beames<br>Date: October 7, 2019<br>Professor Steven Gillette          |  |   |

### Abstract

In this lab, I experimented with a light dependent resistor (LDR) and an LM311 comparator integrated circuit to create a buzzer circuit that can sound a buzzer when the LDR is exposed to light, or to silence the buzzer when the LDR is covered and not exposed to light. Additionally, resistance and voltage values were measured in the circuit to help explain more clearly how the behavior of the circuit is made possible.

### Learning Objectives

- Apply a light dependent resistor in a light detection circuit
- Apply an analog comparator (the LM311) in a light detection circuit
- Measure electrical values using a digital voltmeter

### Notes:

1. Took all voltage measurements relative to ground (unless otherwise stated)
2. Recorded relevant measurements and calculation results in data tables
3. Recorded all measured values on the circuit schematics
4. Used all available precision in calculations, rounded off answers to 3 significant figures

### Materials

| Quantity         | Description                        |
|------------------|------------------------------------|
| 1                | Global Specialties Circuit Trainer |
| 1                | Digital multimeter (DMM)           |
| <b>Circuit 1</b> |                                    |
| 1                | R1 – 2K $\Omega$                   |
| 1                | LDR                                |
| <b>Circuit 2</b> |                                    |
| 1                | Potentiometer, 10k $\Omega$        |
| 1                | Comparator, LM311                  |
| 1                | Piezo buzzer                       |

### Procedure –Circuit 1

1. **Measured and recorded** the resistance value of the light dependent resistor in the full light and in shadow.

| Condition | R <sub>LDR</sub> |
|-----------|------------------|
| Light     | 1.21k $\Omega$   |
| Dark      | 9.54k $\Omega$   |

2. Built Circuit 1

3. **Measured and recorded** the divider voltage output for both light and dark conditions

| Condition | V <sub>out</sub> |
|-----------|------------------|
| Light     | 1.9V             |
| Dark      | 3.93V            |

### Procedure –Circuit 2

4. Built Circuit 2
5. Adjusted the potentiometer until the beeper just turned off
6. **Measured and recorded** comparator input voltages V<sub>1</sub> & V<sub>2</sub> and comparator output voltage V<sub>out</sub>.
7. Shadowed the LDR. The beeper sounded. **Measured and recorded** comparator input voltages V<sub>1</sub> & V<sub>2</sub> and the comparator output voltage.

|       | V <sub>1</sub> | V <sub>2</sub> | V <sub>out</sub> |
|-------|----------------|----------------|------------------|
| Light | 1.99V          | 3.09V          | 312mV            |
| Dark  | 4.24V          | 3.09V          | 3.59V            |

8. Reversed the positions of R1 and the LDR. Adjusted the potentiometer until the beeper just turns on.
9. Shadowed the LDR. The beeper turned off.
10. **Measured and recorded** – V<sub>1</sub>, V<sub>2</sub> and V<sub>out</sub> for light and dark conditions.

|       | V <sub>1</sub> | V <sub>2</sub> | V <sub>out</sub> |
|-------|----------------|----------------|------------------|
| Light | 5.05V          | 2.62V          | 3.59V            |
| Dark  | 4.45V          | 2.63V          | 330mV            |

### Critical Thinking

1. What causes Circuit 1 output voltage to increase in reduced light?

As the amount of light exposed to the light dependent resistor (LDR) decreases, the voltage across the output increases because the resistance increases within the LDR.

2. Describe the change in Circuit 2 output function when R1 and the LDR positions are reversed?

When the light dependent resistor (LDR) is at the bottom of circuit 2, and the 2KΩ resistor is at the top of the circuit, as light increases, resistance decreases across the LDR allowing less voltage to be seen at pin 3 of the LM311 comparator. This input voltage at pin 3 is closer to ground potential and farther away from the voltage seen at pin 2, controlled by the potentiometer. Because of this difference the base of the output

transistor stays low and the beeper is quiet, receiving no voltage from the output transistor's emitter.

When the position of the LDR and the  $2K\Omega$  resistor are changed, the behavior changes. As light increases at the LDR, the voltage across the  $2k\Omega$  resistor increases allowing for the input voltage at pin 3 of the comparator to increase. This increase in voltage then allows the base of the output transistor to reach the threshold voltage to cause the emitter of the output transistor to go high and the beeper sounds.

### 3. Describe a practical application for an LDR.

A light dependent resistor (LDR) has many practical applications. A common household application is external lighting. As the sun goes down, the light across the LDR decreases to a particular threshold and an external household light is then turned on. I have one of these lights at my house.

Additionally, an LDR can be used in robotics applications where a robot could seek out and home in on a light source.

## Conclusions

This lab was an interesting experiment in the behavior of the light dependent resistor (LDR), the behavior of the LM311 comparator as well as a practical application of a voltage divider. As resistance across the LDR decreased, the voltage drop across the component also decreased, forcing the other half of the voltage divider to absorb the majority of the voltage. When connecting to the input pins of the LM311 comparator, this allowed for the control of an output, in this case a buzzer, based on the light allowed into the LDR. The logic could also be reversed so that the buzzer can be either on when light, or on while dark.

## Appendix A – Lab Notes

|                          |  |                                       |
|--------------------------|--|---------------------------------------|
| SIERRA<br>COLLEGE        | MECH 10 - Lab 10<br>Light Activated Switch | Mechatronics<br>Real Skills Real Jobs |
| Name <i>Cayce Beames</i> |  | <i>10/1/19</i>                        |

### Learning Objectives

- Apply a light dependent resistor in a light detection circuit
- Apply an analog comparator (the LM311) in a light detection circuit
- Measure electrical values using a digital voltmeter

### Notes:

1. Take all voltage measurements relative to ground (unless otherwise stated)
2. Record relevant measurements and calculation results in data tables
3. Record all measured values on the circuit schematics
4. Use all available precision in calculations, round off answers to 3 significant figures

### Materials

| Quantity         | Description                        |
|------------------|------------------------------------|
| 1                | Global Specialties Circuit Trainer |
| 1                | Digital multimeter (DMM)           |
| <b>Circuit 1</b> |                                    |
| 1                | R1 – 2K $\Omega$                   |
| 1                | LDR                                |
| <b>Circuit 2</b> |                                    |
| 1                | Potentiometer, 10k $\Omega$        |
| 1                | Comparator, LM311                  |
| 1                | Piezo buzzer                       |

### Procedure –Circuit 1

1. **Measure and record** the resistance value of the light dependent resistor in the full light and in shadow.

| Condition | R <sub>LDR</sub>                |
|-----------|---------------------------------|
| Light     | <i>1.21k<math>\Omega</math></i> |
| Dark      | <i>9.54k<math>\Omega</math></i> |

2. Build Circuit 1
3. **Measure and record** the divider voltage output for both light and dark conditions

| Condition | V <sub>out</sub> |
|-----------|------------------|
| Light     | <i>1.9V</i>      |
| Dark      | <i>3.93V</i>     |

### Procedure –Circuit 2

4. Build Circuit 2
5. Adjust the potentiometer until the beeper just turns off
6. **Measure and record** comparator input voltages  $V_1$  &  $V_2$  and comparator output voltage  $V_{out}$ .
7. Shadow the LDR. The beeper should sound. **Measure and record** comparator input voltages  $V_1$  &  $V_2$  and the comparator output voltage.

|       | $V_1$ | $V_2$ | $V_{out}$ |
|-------|-------|-------|-----------|
| Light | 1.99V | 3.09V | 3.12mV    |
| Dark  | 4.24V | 3.09V | 3.59V     |

8. Reverse the positions of R1 and the LDR. Adjust the potentiometer until the beeper just turns on.
9. Shadow the LDR. The beeper should turn off.
10. **Measure and record** –  $V_1$ ,  $V_2$  and  $V_{out}$  for light and dark conditions.

|       | $V_1$ | $V_2$ | $V_{out}$ |
|-------|-------|-------|-----------|
| Light | 5.05V | 2.62V | 3.59V     |
| Dark  | 4.45V | 2.63V | 3.30mV    |

### Critical Thinking

1. What causes Circuit 1 output voltage to increase in reduced light? *Resistance increases*
2. Describe the change in Circuit 2 output function when R1 and the LDR positions are reversed? *Resistance relative to ground is opposite.*
3. Describe a practical application for an LDR. *alarm, switch to cause motor to work light following robot.*

### Grading Criteria

|                          |  | Points Possible | Points Earned |
|--------------------------|--|-----------------|---------------|
| <b>Documentation</b>     | Abstract, introduction, experiment, data results, conclusions, attachments, clarity, spelling, grammar | 10              |               |
| <b>Circuit 1</b>         | Resistance values and divider voltage values and recorded in data table                                | 5               |               |
| <b>Circuit 2</b>         | Comparator input and output voltages accurate and recorded in data table                               | 5               |               |
|                          | Comparator input and output voltages accurate and recorded in data table (with R1 & LDR reversed)      | 5               |               |
| <b>Critical Thinking</b> | Questions answered completely & accurately. State conclusions drawn and lessons learned from the lab   | 10              |               |
| <b>On-time submittal</b> | Lab report is submitted in accordance with the assignment due date as posted on Canvas                 | 5               |               |
| <b>Total</b>             |  | <b>40</b>       |               |





### Light Dependent Resistor (LDR)


Light dependent resistors will provide variable resistance as a function of light intensity. More intense light reduces resistance. They are made from cadmium-sulfide. In this circuit, the LDR serves as one resistance in a two-resistor voltage divider causing output voltage to increase as light intensity decreases.

### LM311 Comparator

The LM311 comparator output is an NPN transistor connected between pins 1 and 7. In this circuit the output transistor sources current to the piezo buzzer from the collector on pin 7 to the emitter on pin 1. Switching action is driven by a comparison of the pin 2 & 3 voltage values. Output is high when Pin 3 exceeds the Pin 2 reference voltage.

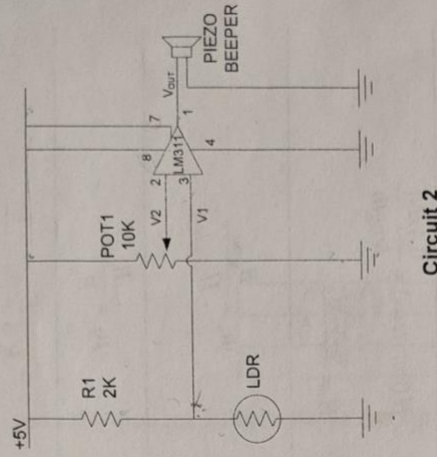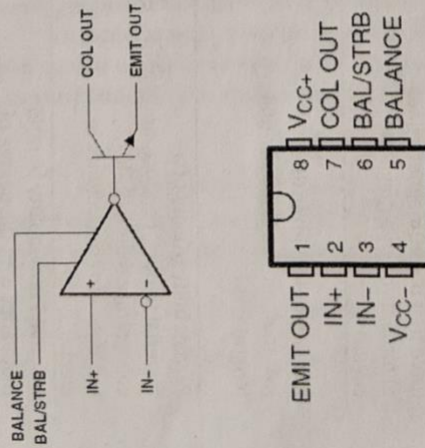

Circuit 1

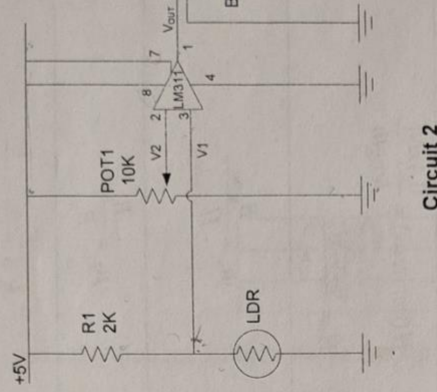

Circuit 2

|  |         |                                       |        |
|--|---------|---------------------------------------|--------|
| SIERRA COLLEGE                               |         | MECH 10 – FUNDAMENTALS OF ELECTRONICS |        |
| Mechatronics<br><i>Real Skills Real Jobs</i> |         | LAB 10 – LIGHT OPERATED SWITCH        |        |
| SIZE   | FSCM NO | DWG NO                                | REV    |
|  |         | MECH10-10                             | 0.1    |
| SCALE  | NONE    | SHEET                                 | 1 OF 1 |
| DRAWN BY – SDG                               |         |                                       |        |
| JULY 2011                                    |         |                                       |        |

**Grading Criteria**

|                          |  | <b>Points Possible</b> | <b>Points Earned</b> |
|--------------------------|--|------------------------|----------------------|
| <b>Documentation</b>     | Abstract, introduction, experiment, data results, conclusions, attachments, clarity, spelling, grammar | <b>10</b>              |                      |
| <b>Circuit 1</b>         | Resistance values and divider voltage values and recorded in data table                                | <b>5</b>               |                      |
| <b>Circuit 2</b>         | Comparator input and output voltages accurate and recorded in data table                               | <b>5</b>               |                      |
|                          | Comparator input and output voltages accurate and recorded in data table (with R1 & LDR reversed)      | <b>5</b>               |                      |
| <b>Critical Thinking</b> | Questions answered completely & accurately. State conclusions drawn and lessons learned from the lab   | <b>10</b>              |                      |
| <b>On-time submittal</b> | Lab report is submitted in accordance with the assignment due date as posted on Canvas                 | <b>5</b>               |                      |
|                          | <b>Total</b>   | <b>40</b>              |                      |

## **Lab Report Format**

**Abstract** - a summary and high-level overview of the lab and its results

**Introduction** - State the objectives of the laboratory and list the equipment required

**Experiment** - Describe the procedure used to carry out the lab

**Results Data** - list data taken in table or graphical format where appropriate

**Critical Thinking** - State the conclusions drawn and lessons learned from the laboratory activities. Answer any questions found within the lab procedure.

**Attachments** – grading criteria, verification signatures, circuit diagrams, lab procedures & notes