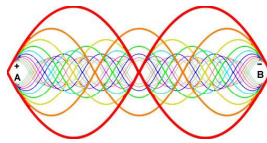


## Class 16


### Reactive Components V
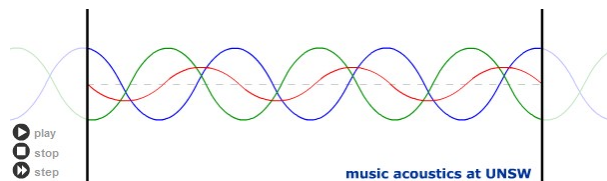
### Resonance



1



- Resonance
  - The tendency of a system to increase the amplitude of oscillation for certain frequencies



2

- Resonance

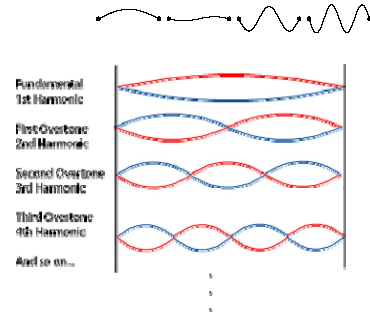
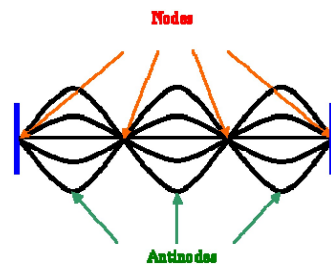
- The tendency of a system to increase the amplitude of oscillation for certain frequencies



3



- Resonance

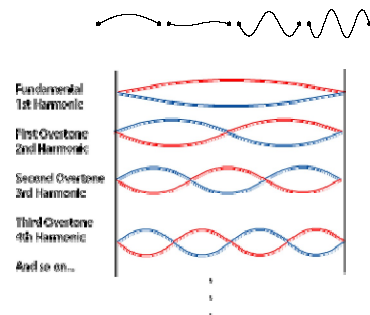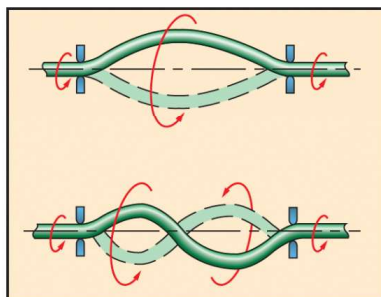- The tendency of a system to increase the amplitude of oscillation for certain frequencies






4

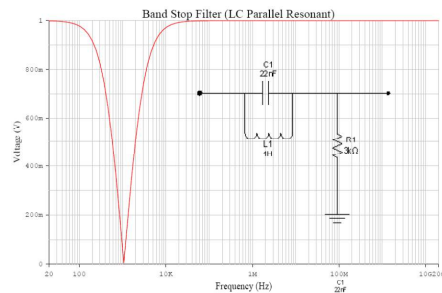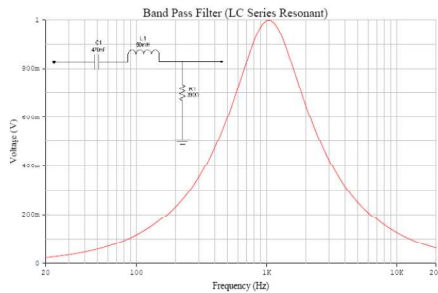- Electrical Resonance
  - The tendency of a circuit to increase the amplitude of oscillation for certain frequencies
  - Electrical nodes & anti-nodes




5

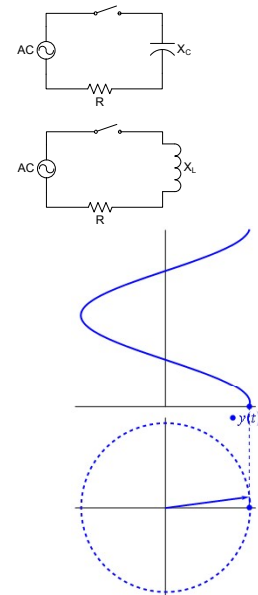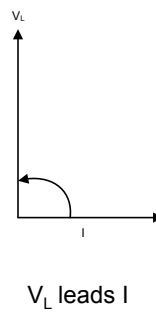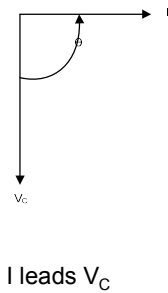- Electrical Resonance
  - Series RL & RC Phasor Diagrams
    - Constant current reference
    - Variable voltage & impedance




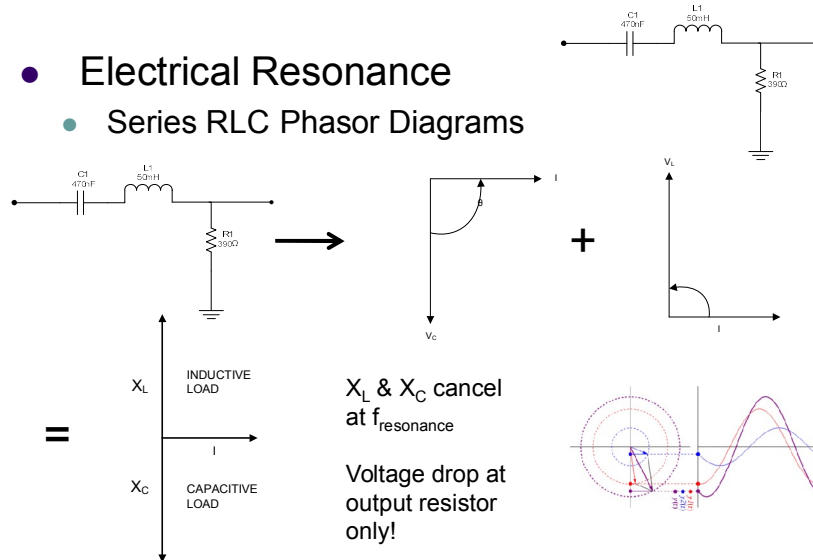- Electrical Resonance
  - Series RLC Phasor Diagrams







7

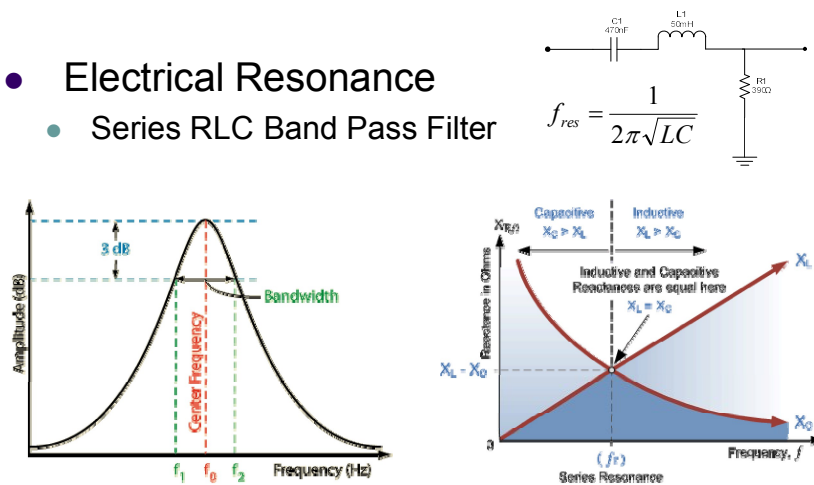- Electrical Resonance
  - Series RLC Band Pass Filter







8

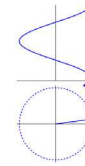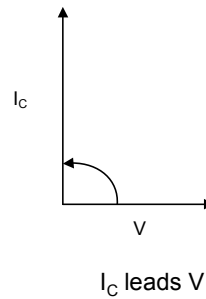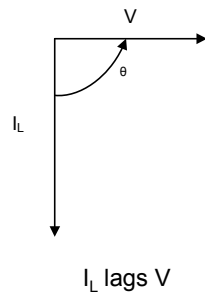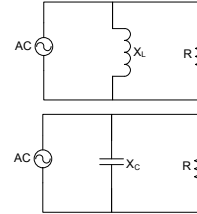- Electrical Resonance
  - Parallel RL & RC Phasor Diagrams
    - Constant voltage reference
    - Variable current through branches




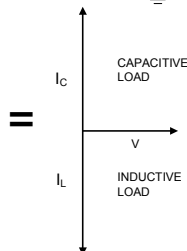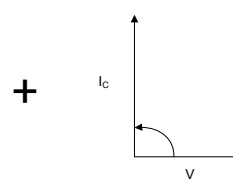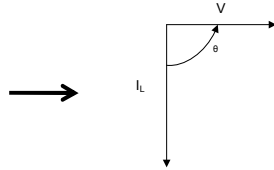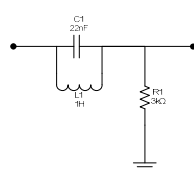- Electrical Resonance
  - Parallel RLC Phasor Diagrams



$I_L$  &  $I_C$  cancel  
at  $f_{\text{resonance}}$



Voltage drop at  
tank circuit  
only!

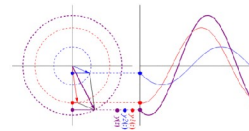

10

- Electrical Resonance
  - Parallel RLC Band Stop Filter

$$f_{res} = \frac{1}{2\pi\sqrt{LC}}$$

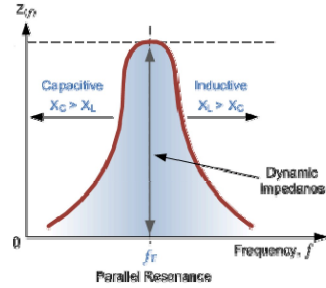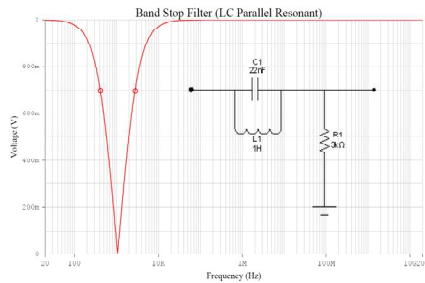

11

## Lab 16 – Resonance

### Learning Objectives

- Simulate and test circuits using circuit analysis software
- Create Bode plots of RLC frequency performance
- Analyze band pass filter performance
  - Cutoff frequency
  - Bandwidth

		Points Possible
Documentation	Quality of documentation (neatness, clarity, spelling, grammar), Expected and measured values recorded on schematic diagram	10
Band Stop Filter	Bode plot reviewed & signed, bandwidth, $X_L$ , $X_C$ , $f_{CO}$ , calculated and recorded in data table	10
Band Pass Filter	Bode plot reviewed & signed, bandwidth, $X_L$ , $X_C$ , $f_{CO}$ , calculated and recorded in data table	10
Conclusions	Questions answered completely & accurately.	20
	<b>Total</b>	<b>45</b>

12