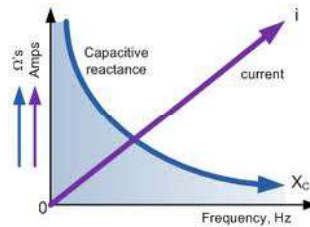


Class 14

Reactive Components III


Capacitive Reactance




http://www.electronics-tutorials.ws/capacitor/cap_8.html

1

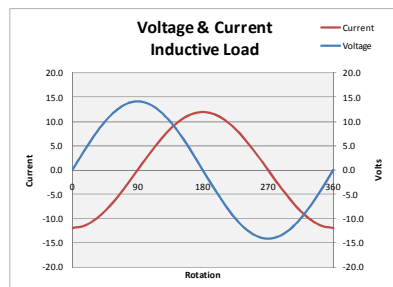- Reactance
 - The opposition to changes in current or voltage



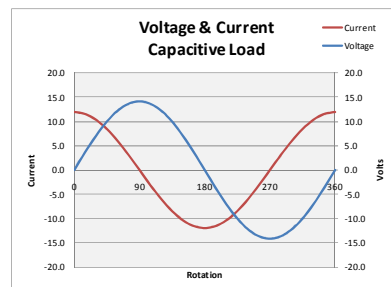Opposes Current Change
Voltage Leads Current



Opposes Voltage Change
Current Leads Voltage

2

- Capacitive Reactance

- A capacitor's opposition to changes in voltage
- Characteristics
 - Inversely proportional to frequency & capacitance
 - A frequency dependent resistor
- Applications
 - Motor starting circuits
 - Frequency filters

$$X_C = \frac{1}{2\pi fC}$$

Where;

X_C = capacitive reactance (Ω)

$2\pi f$ = angular velocity (rad/sec)

f = frequency (Hz)


C = capacitance (F)

Name	Unit symbol	Quantity	Symbol
capacitive reactance	X_C	Ohms	Ω

3

- Capacitive Reactance


- Circuit Examples
 - Find X_C

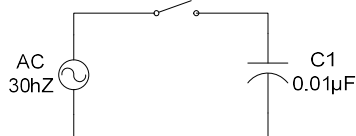

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{2\pi \times 30 \times 0.01\mu F}$$

$$X_C = ???\Omega$$

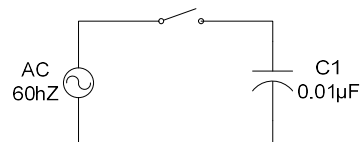

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{2\pi \times 60 \times 0.01\mu F}$$



$$X_C = ???\Omega$$

4

Capacitive Reactance

Impedance

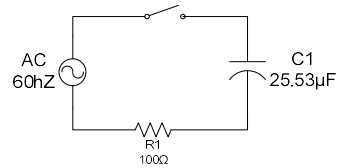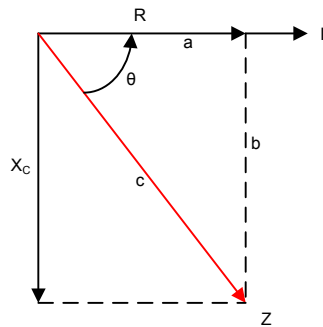- $R_T \neq X_C + R_1$
- Vector addition required
- Pythagorean Theorem



$$X_C = \frac{1}{2\pi fC} = 104\Omega$$

$$R_1 = 100\Omega$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{100^2 + 104^2}$$


$$Z = ??\Omega$$

5

Capacitive Reactance

Impedance – the total opposition to current flow in an AC circuit

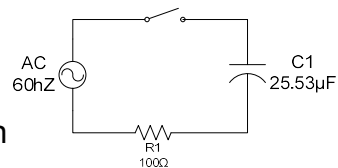- Resistance & Reactance
 - Vector addition
- For all reactive circuits!



$$X_C = \frac{1}{2\pi fC} = 104\Omega$$

$$R_1 = 100\Omega$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{100^2 + 104^2}$$


$$Z = ??\Omega$$

Name	Unit symbol	Quantity	Symbol
impedance	Z	Ohms	Ω

6

- Capacitive Reactance
 - Frequency Filters
 - High Pass Filters – Series RC

**Frequency
dependent
resistor!**

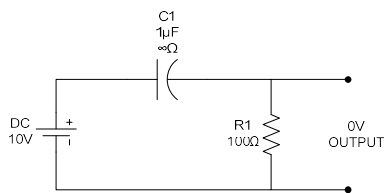

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{2 \times \pi \times 0 \times 1\mu F}$$


$$X_C = \infty(\text{undefined})$$

7

- Capacitive Reactance
 - Frequency Filters
 - High Pass Filters – Series RC

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 1592 \times 1\mu F}$$

$$X_C = ??\Omega$$

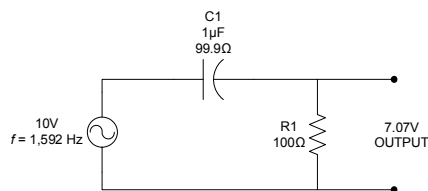

Half power point – the frequency where the output is at ½ total circuit power

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{100^2 + 99.97^2} = ??\Omega$$

$$I_T = \frac{V_S}{Z} = \frac{10V}{141.3\Omega} = ??mA$$

$$V_{R1} = I_T \times Z$$

$$V_{R1} = 70.77mA \times 100\Omega$$


$$V_{R1} = ??V$$

SDG

8

- Capacitive Reactance

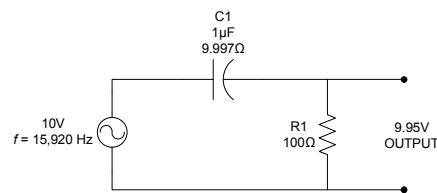- Frequency Filters
 - High Pass Filters – Series RC



$$X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 15,920 \times 1\mu F}$$

$$X_c = ??\Omega$$

$$Z = \sqrt{R^2 + X_c^2}$$

$$Z = \sqrt{100^2 + 9.997^2} = ??\Omega$$

$$I_T = \frac{E}{Z} = \frac{10V}{100.5\Omega}$$

$$I_T = ??A$$

$$V_{R1} = 0.995A \times 100\Omega$$

$$V_{R1} = ??V$$


SDG

9

- Capacitive Reactance

- Frequency Filters
 - High Pass Filters – Series RC

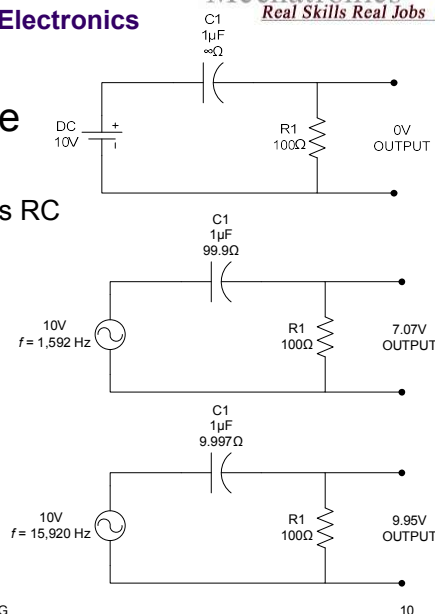A high-pass filter allows high frequencies to pass through the filter relatively unaffected, while greatly attenuating (preventing) low frequencies from reaching the output.




SDG

10

- Capacitive Reactance
 - Frequency Filters
 - Low Pass Filters – Series RC

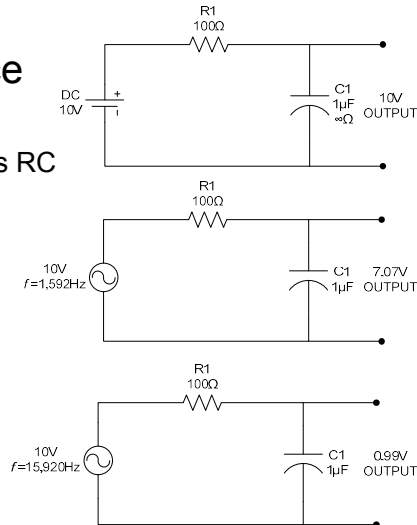A low-pass filter allows low frequencies to pass through the filter relatively unaffected, while greatly attenuating (preventing) high frequencies from reaching the output.



SDG

11

● Lab 14 – High & Low Pass Filters

Learning Objectives

- Build and test the output of a high pass filter (series RC)
- Test the circuit output characteristics with different capacitance values
- Build and test the output of a low pass filter (series LC)
- Test the circuit output characteristics with different inductance values
- Create frequency response curves (Bode Plots) using Electronic Workbench

		Points Possible
Documentation	Quality of documentation (neatness, clarity, spelling, grammar). Expected and measured values recorded on schematic diagram	10
X _c and Resistor Calculations	Values calculated and accurate, work is shown	5
High Pass Filter	Filter impact on frequencies recorded & accurate	5
	Changes to circuit performance noted with new capacitance value added	5
Low Pass Filter	Filter impact on frequencies recorded & accurate	5
	Changes to circuit performance noted with new inductance value added	5
Frequency Response Curves	Response curves (4) included and accurate	5
Conclusions	Questions answered completely & accurately.	10
SDG Total		50

12